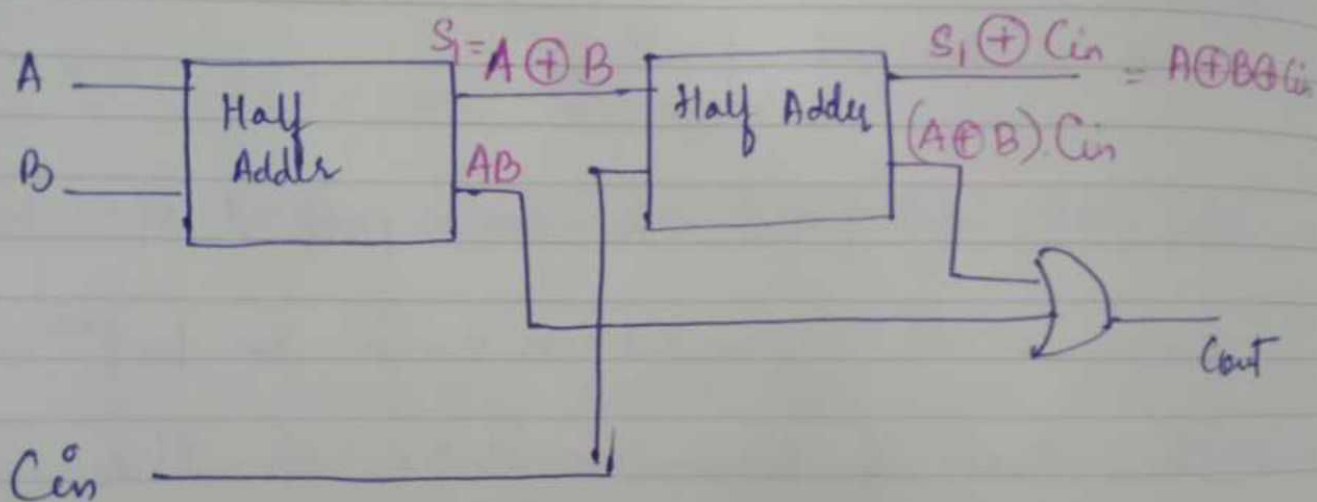


31

SATURDAY • AUGUST

COMBINATIONAL CIRCUITSFull Adder using Half Adder:-

* If full adder not available & we have only half adders, we can design full adder using two half adders.

Half Adder

$$S_1 = A \oplus B$$

$$Carry_1 = A \cdot B$$


$$C_{out} = (A \oplus B) C_{in} + AB$$

$$A + \bar{A}B$$

$$= A + B$$

COMBINATIONAL CIRCUITSFull Adder using Half Adder:-

* If full Adder not available & we have only half adders, we can design full Adder using two half Adders.

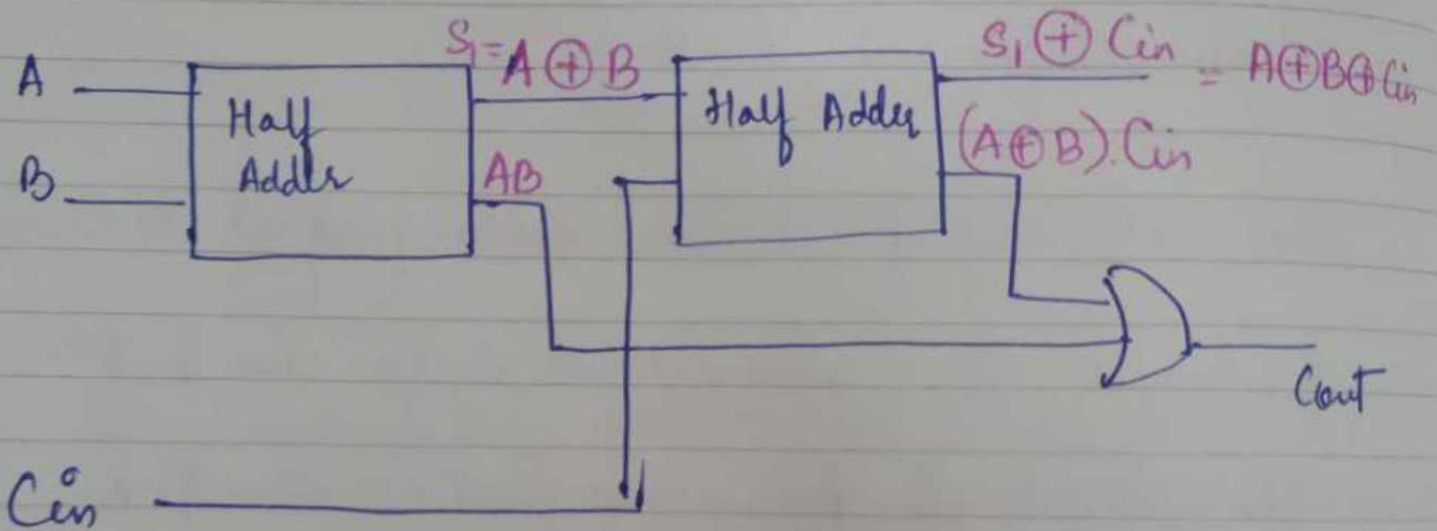Half Adder

$$S_1 = A \oplus B$$

$$Carry_1 = A \cdot B$$

$$A + \bar{A}B$$

$$= A + B$$

$$C_{out} = (A \oplus B) C_{in} + AB$$

$$= (\bar{A}B + A\bar{B}) C_{in} + AB$$

$$= \bar{A}B C_{in} + A\bar{B} C_{in} + AB$$

$$= B(\bar{A} C_{in} + A) + A\bar{B} C_{in}$$

$$= B(A + C_{in}) + \bar{B}A C_{in}$$

01

SUNDAY • SEPTEMBER

$$= AB + BC_{in} + \bar{B}AC_{in}$$

$$= AB + BC_{in} + \bar{B}A(B + \bar{B})C_{in}$$

$$= AB + (A + B)C_{in}$$


$$= \underline{AB + BC_{in} + C_{in}A}$$

Self study
Subtractors

N Bit parallel Adder :-

- ↳ cascade of Full Adders
- ↳ device for adding multi bit nos.

4-bit Parallel Adder :-

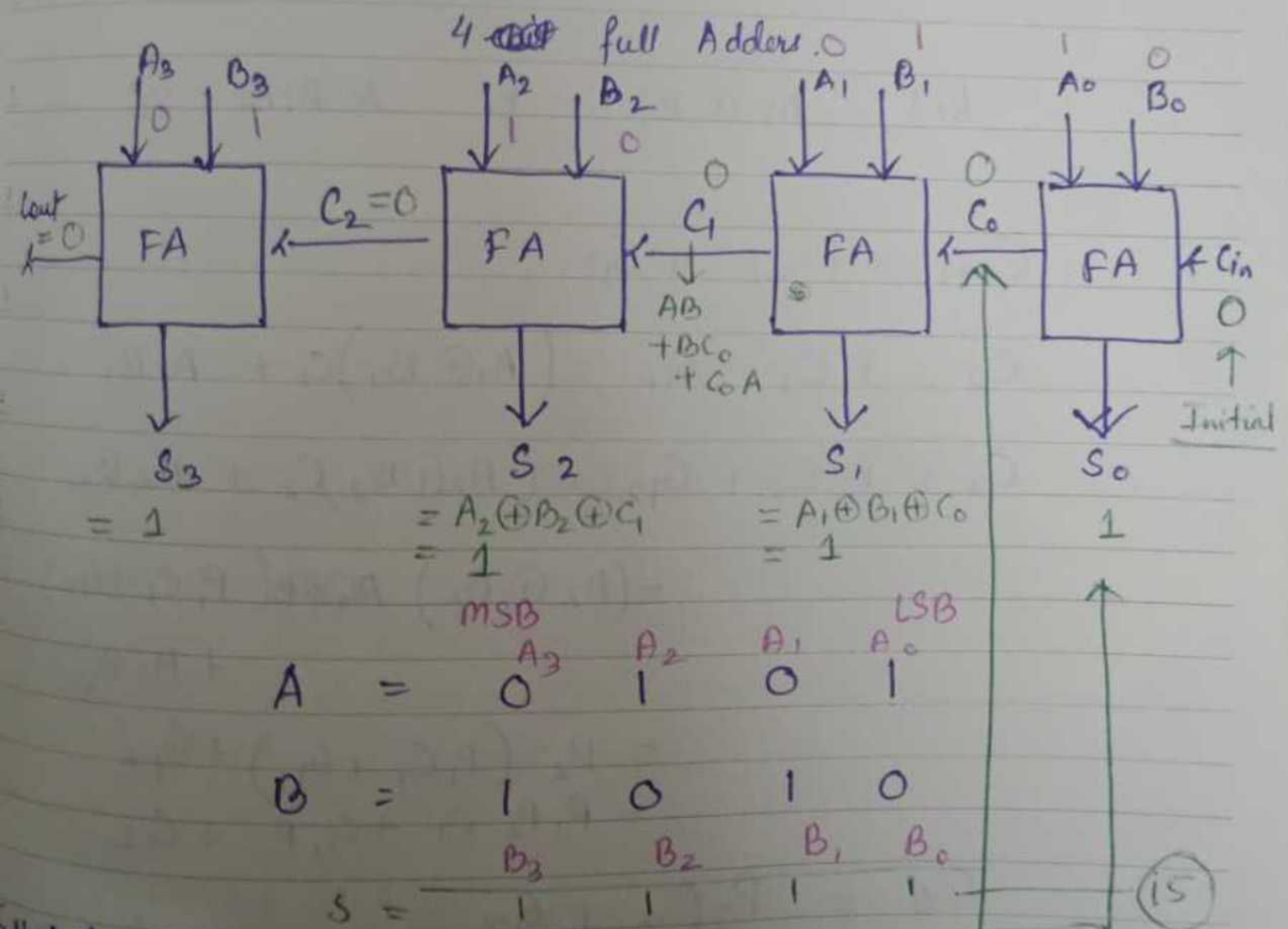

Full Adder: -
 Sum = $A \oplus B \oplus C$
 Carry = $AB + BC + CA$