

COMBINATIONAL CIRCUITS

↳ output is dependent upon combination of input variables.

↳ Does not use any memory.

↳ It can have ' n ' no. of inputs & ' m ' no. of outputs.

↳ eg:- Adders & Subtractors

Decoders

Comparators

MUX


Code Converters

ROM

PLA

PAL

i/p

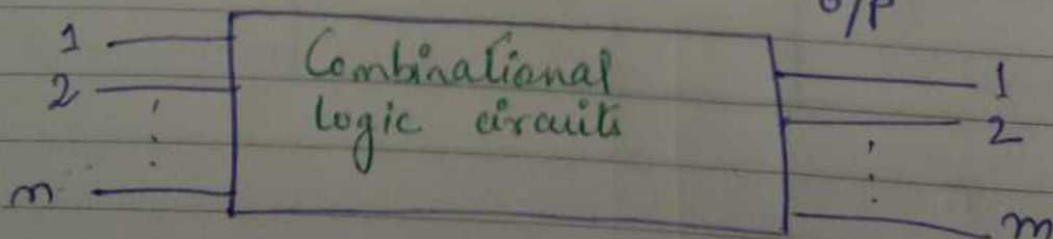

COMPARISON BETWEEN COMBINATIONAL & SEQUENTIAL CKTS

Combinational

↳ O/p is dependent on the present input

↳ ex: Adder


$$\begin{array}{r} 1 \\ + 0 \\ \hline 1 \end{array}$$


Sequential

↳ O/p depends on the present i/p as well as previous O/p or O/p's

↳ Counter (ex)

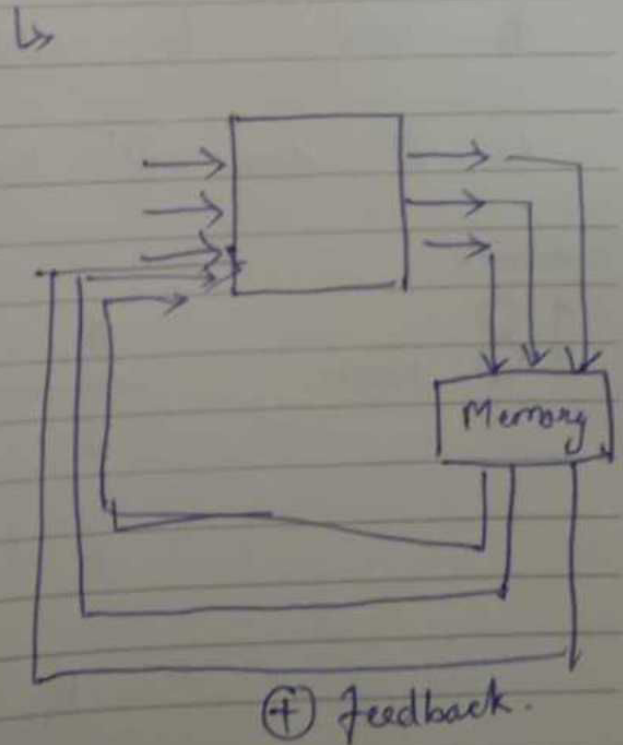+1 to the previous O/p
If O/p is 5 that means previous O/p was 4 to which 1 is added



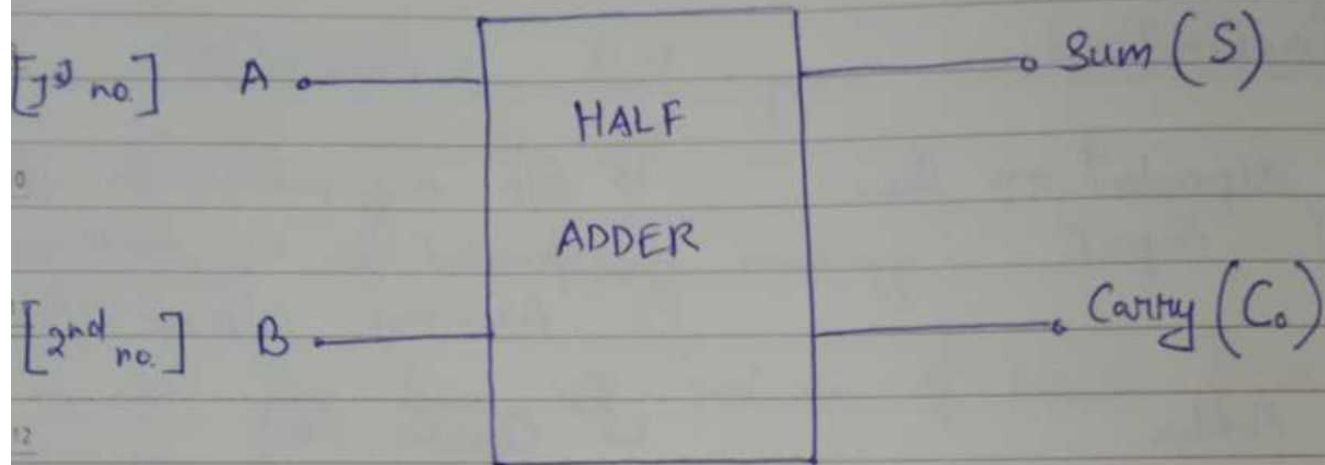HALF ADDER

$$S = A \oplus B$$

$$C_o = A \cdot B$$


→ used to add a single bit nos.


→ It does not take carry from previous sum.

A	B	S	C _o
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

} Binary
Addition
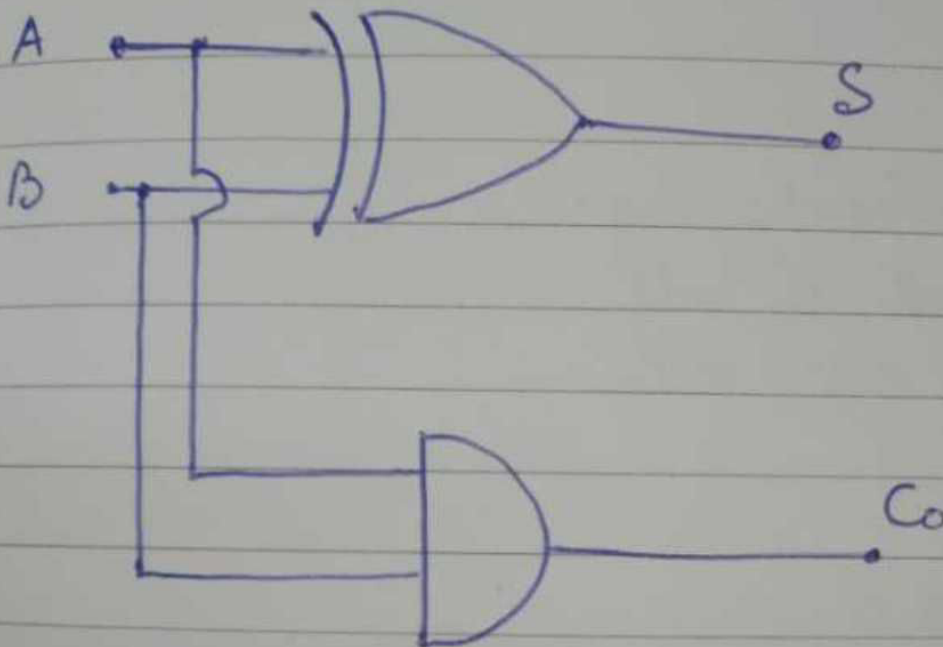
$$\begin{aligned} S &= A \oplus B \\ C_o &= A \cdot B \end{aligned}$$



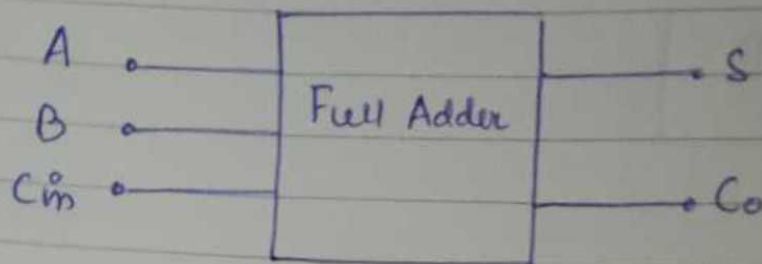FULL ADDER :-

11 \Rightarrow Full Adder is a arithmetic logic circuit ~~dog~~ designed to add two single bit nos. with a carry.

$$\begin{array}{r}
 A \quad 0 \quad 0 \\
 B \quad 0 \quad 1 \\
 C \quad 0 \quad 1 \\
 \hline
 \quad 1 \quad 0 \\
 \quad \quad 0
 \end{array}$$

4 T.T.

A	B	Cin	S	Co
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Sum

Checkboard configuration

A \ BCin				
	00	01	11	10
0	0	1	0	1
1	1	0	1	0

$$S = A \oplus B \oplus C_{in}$$

Carry out

A \ BCin				
	00	01	11	10
0	0	0	1	0
1	0	1	1	1

$$C_o = BC_{in} + AB + AC_{in}$$

$$C_o = AB + BC_{in} + C_{in}A$$

