

Date  
27/09/21

### Classwork

① Which of the following(s) cannot be used as inverter?

Ⓐ NAND , ~~Ⓑ AND~~ , Ⓒ NOR , Ⓓ XOR

Ans:- Ⓑ AND

② A gate is enabled when its enable input is at logic 1. The gate is:-

Ⓐ OR , ~~Ⓑ NAND~~ , Ⓒ NOR , Ⓓ NONE

Ans:- Ⓑ NAND

③ The output of logic gate is 1, When all its inputs are at logic 1. The gate is either

- (a) a NAND or a NOR, (b) an AND or an XNOR  
(c) an OR or a NAND, (d) an XOR or an XNOR

Ans: (b) an AND or an XNOR

④ The no. of rows in the truth table of a 4-input gate is

- (a) 4 (b) 8 (c) 12 (d) 16

Ans: (d) 16

⑤ For the gate shown in the figure, the output will be HIGH



- (a) if both inputs are HIGH  
(b) if one of the inputs is HIGH  
(c) if one of the inputs is LOW  
(d) if and only if both the inputs are LOW.

Ans: (b) if one of the inputs is HIGH.

⑥ Consider the expression  $Z = A \oplus B \oplus C$ , where A, B, C are input variables and Z is the output variable. Z will be logic 1 if

- (a) an even no. of input variables are 1  
(b) an odd no. of input variables are 1  
(c) an even no. of input variables are 0  
(d) an odd no. of input variables are 0

Ans: (b) an odd no. of input variables are 1.

⑦ The X-OR and X-NOR gates can have how many inputs?

- ☒ (a) 2      (b) 1      (c) 4      (d) any number

Ans:- (a) 2

⑧ The logic expression  $AB + \bar{A}\bar{B}$  can be implemented by giving the input A and B to a two input

- (a) NOR gate      (b) NAND gate      (c) X-OR gate      ☒ (d) X-NOR gate

Ans:- (d) X-NOR gate