

NUMBER SYSTEM (contd...)

9's and 10's complement:-

- Subtraction of decimal no. can be obtained by the 9's and 10's complement methods ~~similar~~
- The 9's complement of decimal no. obtained by subtracting each digit of that decimal no. from 9.
- 10's complement \rightarrow adding 1 to its 9's comp.

e.g.:- 9's complement :-

3465

$$\begin{array}{r} 9 9 9 9 \\ - 3 4 6 5 \\ \hline 6 5 3 4 \end{array}$$



9's complement of 3465

17

WEDNESDAY • APRIL

2019 - MARCH

S	M	T	W	T	F	S
31						
3	4	5	6	7		
10	11	12	13	14		
17	18	19	20	21	22	
24	25	26	27	28	29	

10's complement
4069

✓

$$\begin{array}{r}
 9999 \\
 - 4069 \\
 \hline
 5930 \leftarrow 9\text{'s comp. of } 4069
 \end{array}$$

$$\begin{array}{r}
 + 1 \\
 \hline
 5931 \leftarrow 10\text{'s comp. of } 4069
 \end{array}$$

✓

1056 · 074

$$\begin{array}{r}
 9999. 999 \\
 - 1056. 074 \\
 \hline
 8943. 925 \\
 + 1 \\
 \hline
 8943. 926
 \end{array}$$

9's complement Method of subtraction:-

- ↳ Obtain The 9's complement of the subtrahend and add it to the minuend.
- ↳ If there is a carry, it indicates the answer is positive. Add the carry to the LSD of the result to get the answer. This is called end around carry.
- ↳ If there is no carry, the ans is -ve. and the intermediate result is its 9's complement. Take the 9's complement of this result & place a -ve sign in front to get the ans.

eg:-

$$\begin{array}{r} 745.81 \\ - 436.62 \\ \hline \end{array} \Rightarrow + \begin{array}{r} 745.81 \\ 563.37 \\ \hline \end{array} \quad (9's \text{ comple. of } 436.62)$$

$\textcircled{1} \ 309.18 \quad (\text{Intermediate result})$

$\swarrow + 1$

$\underline{\underline{309.19}} \quad (\text{Ans.})$

Carry \rightarrow the ans.

$$\therefore \text{Ans.} - + \underline{309.19}$$

$$\begin{array}{r} 436.12 \\ - 745.81 \\ \hline \end{array} \Rightarrow + \begin{array}{r} 436.62 \\ 254.18 \\ \hline \end{array} \quad (9's \text{ comple. of } 745.81)$$

$\underline{\underline{690.80}}$ \downarrow $(\text{Intermediate result, no carry})$

9's complement is 309.19

$$\therefore \text{Ans.} - \underline{309.19}$$

APRIL • SATURDAY

20

20 22 23 24 25 26
28 29 30 31

10's complement method of Subtraction:-

- ↳ Obtain 10's complement of the subtrahend & add it to the minuend.
- If carry, ignore
- If carry, ans is +ve; the result obtained itself is the ans.
- If no carry, ans is -ve, the result obtained is its 10's complement.

22

MONDAY • APRIL

12 13 14
17 18 19 20 21 22
24 25 26 27 28 29

Representation of Signed Nos:-

① Signed magnitude form.

② Complement form [$\rightarrow 1's$, $\rightarrow 2's$]

7 \rightarrow 111

+7 or -7 \rightarrow ? , '+' \rightarrow 0
'-' \rightarrow 1.

Signed Magnitude form :-

Syntax :- [Sign Bit | Actual Binary]

eg: +7 [0 | 111]

-7 [1 | 111]

Complement Form :-



1's complement.

2's complement.

→ Complementing each & every digit of
binary decimal no.

$$9 \rightarrow 1001$$

↓ 1's comp.

$$0110$$

→ Adding 1 to 1's complement.

$$9 \rightarrow 1000$$



0110 (1's complement)


$$+ 1$$

$$0111 \text{ (2's complement)}$$

1's complement Representation of signed no:-

Syntax:-

Sign bit	1's complement of actual binary
----------	------------------------------------

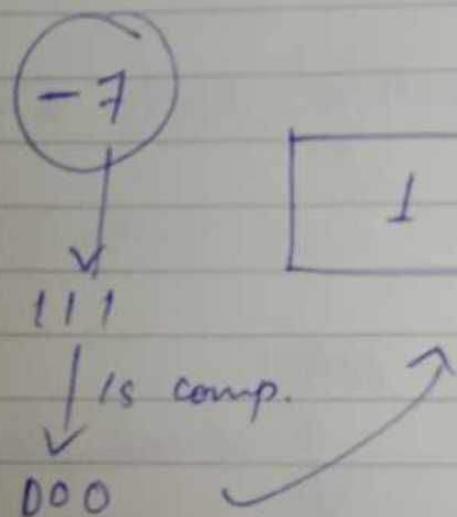

2's comp.
Representation Syntax:-

Sign bit	2's complement of actual binary
----------	------------------------------------

$$\begin{array}{l} \text{Q} \rightarrow \frac{-7}{\overline{111}} \rightarrow \\ \text{1's} \rightarrow 000 \\ \text{2's} \rightarrow +1 \\ \hline 001 \end{array}$$

1	001
---	-----

2's complement Subtraction:-

- ↳ Add 2's complement of the subtracted to the minuend.
- ↳ If there is carry out, ignore it.
- ↳ Look at sign bit, i.e MSB of the sum term, If MSB is '0' result is +ve & if it is ~~'0'~~ result is -ve and is in its 2's complement form.
- ↳ Take its 2's complement to find its magnitude in binary.

Ex:- Subtract 14 from 46 using
8 bit 2's complement arithmetic.

$$\begin{array}{r} +14 \\ \hline 0000\ 1110 \\ 1111\ 0010 \end{array}$$

Ex:- $48 - 28$

$$48 + (-28)$$

2's complement of 28

$$48 \rightarrow 110000$$

$$28 \rightarrow 011100$$

↓ , ,

$$1's\ Comp \rightarrow 100011$$

+1

$$\rightarrow \overline{100100}$$

$$+110000$$

① 010100

Discard


JUNE - 2019

M	T	W	T	F	S	S
3	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28	29	30

WK 21 (141-224)

MAY • TUESDAY

21

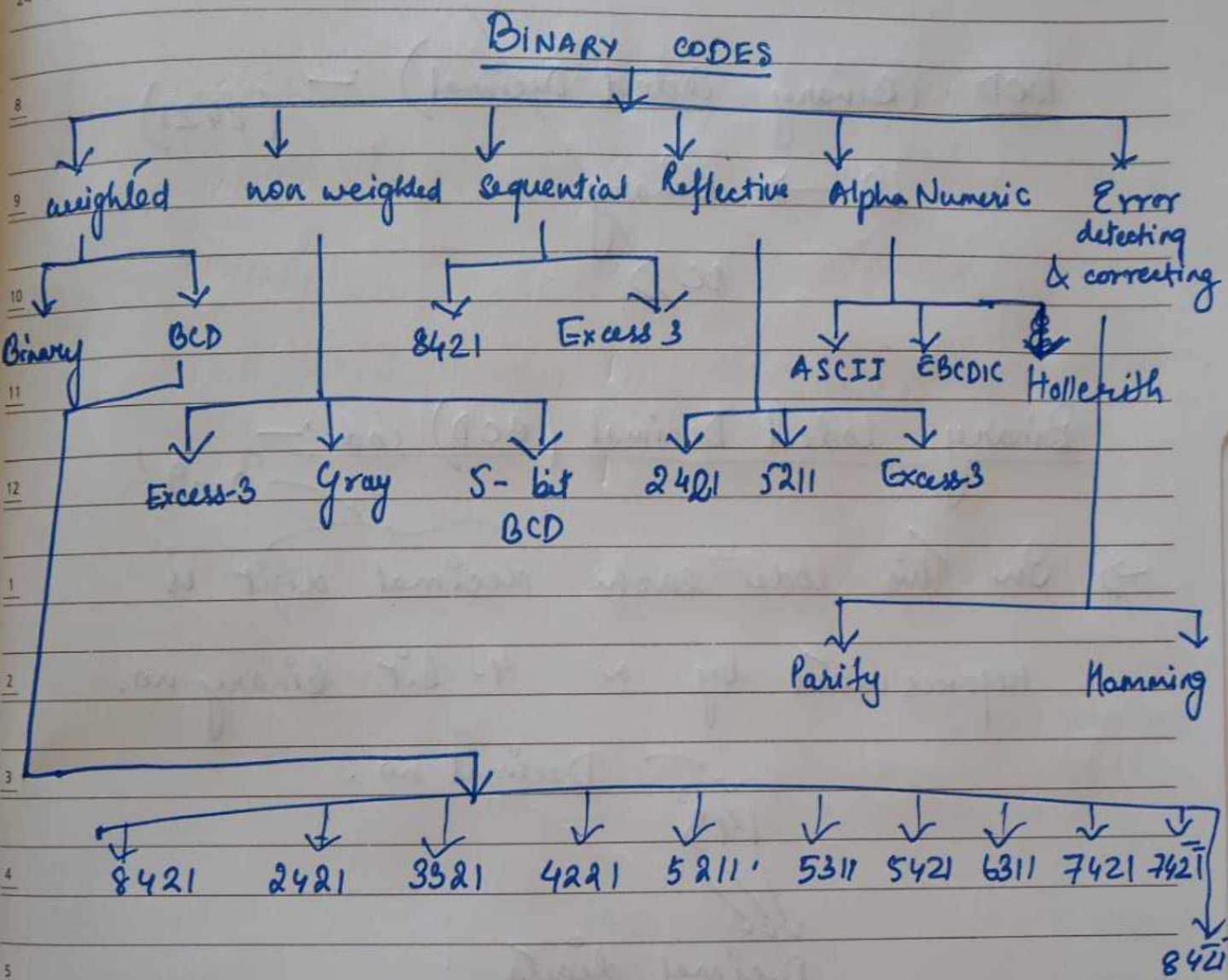

Binary Loded Decimal (BCD) code - '0-9'

→ In this code each decimal digit is represented by a 4-bit binary no.

143
↓↓↓
Decimal digits .

→ Positional weights are '8,4,2,1', so also called 8421 code.

Decimal

0

1

2

3

4

5

6

7

8

9

BCD

0 0 0 0

0 0 0 1

0 0 1 0

0 0 1 1

0 1 0 0

0 1 0 1

0 1 1 0

0 1 1 1

1 0 0 0

1 0 0 1

$$4 \text{ bits} - 2^4 = 16$$

Invalid
Oct

10

11

12

13

as

14

they
are

15

decimal
no. & not decimal
digits

x x x x

x x x x

,

,

.

.

x x x x

↳ Conversion of Decimal No to BCD.

(i) $(17)_{10} \Rightarrow 00010111$

1 7

0001 0111

(ii) $156 \Rightarrow ?$

↳ BCD to Decimal :-

(i) 10100 BCD

0001 0100
1 4

(14)₁₀

Make group
of 4 bits
from right.

1	2					
3	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28	29	30

MAY • SATURDAY

25

(ii) 10010 01

0100 1001

$(49)_{10}$

↳ Comparison betn Binary & BCD :-

$(10)_{10} \rightarrow$ Binary 1010 BCD 0001 0000

$(12)_{10} \rightarrow$ 1100 0001 0010

27

MONDAY • MAY

1	2	3	4	5	6
7	8	9	10	11	12
14	15	16	17	18	19
21	22	23	24	25	26

BCD Addition:

- 1) Sum ≤ 9 , final carry = 0 | Ans ✓
- 2) Sum ≤ 9 , final carry = 1 | Ans ✗ (To correct it add 0110)
- 3) sum > 9 , final carry = 0 | Ans ✗ ("")

Perform
Simple binary
addition.

✓ $(2)_{10} + (6)_{10}$

$$\begin{array}{r}
 0010 \\
 0110 \\
 \hline
 1000
 \end{array}
 \begin{array}{l}
 \text{Sum} < 9 \\
 \text{Final carry} = 0.
 \end{array}$$

✓ $(3)_{10} + (7)_{10}$

$$\begin{array}{r}
 0011 \\
 0111 \\
 \hline
 1010
 \end{array}
 \begin{array}{l}
 \text{Sum} > 9 \\
 \text{Final carry} = 0
 \end{array}$$

We have to add 0110.

$$2^4 = 16$$

0 0
:
:
:
:
:
:
9 15

$$15 - 9 = 6$$

Sum = 1010 → Binary


$$\begin{array}{r} 000 \\ + 10000 \\ \hline 10 \end{array}$$

K-Map :- (Karnaugh Map).

→ Developed by Karnaugh in 1953

→ Used to simplify boolean algebraic expressions without using Boolean laws.


2-variable K-Map.

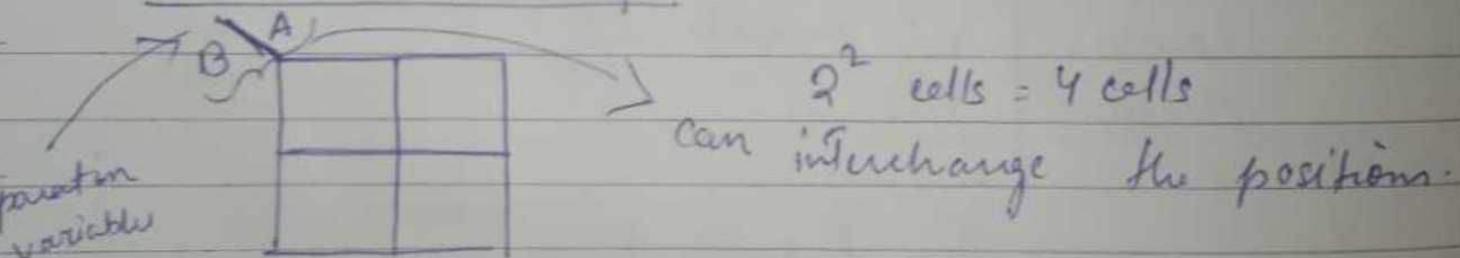

2nd "number of cells = 2"

n = no. of variables.

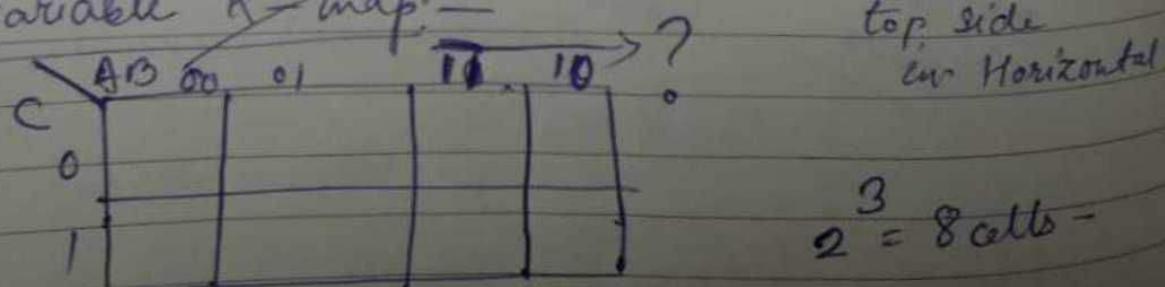3 variable K-map:— → maximum variables at top side over Horizontal



Horizontal representation

	A	0	1
BC	00		
	01		
	11		
	10		

Vertical representation.

4-variable K-Map:-

$$2^4 = 16 \text{ cells.}$$

	CD	00	01	11	10
AB	00				
	01				
	11				
	10				

slice slice slice slice

WEEK 27 (188-177)

SUNDAY

$$ABCD = 1111$$

$$ABCD = 0111$$

07

AUGUST

Rules for K-Map Simplification:-

9. 1. Groups may not contain zero.

2. We can group 1, 2, 4,
11 8 (or) 2^n cells.

- 12 3. Each group should \rightarrow prime implicant.
be as large as possible

4. cells containing I must
be grouped

5. Groups may overlap.

- ⁴ 6. Opposite grouping and corner grouping is allowed.

7. There should be as few groups as possible.

For SOP, ~~so~~ groups may not contain 0.


group single variable

2 " 1


Octal (8 variables)

5 6 7 8 9 10 11 12
 13 14 15 16 17 18
 19 20 21 22 23 24 25
 26 27 28 29 30 31

JULY TUESDAY

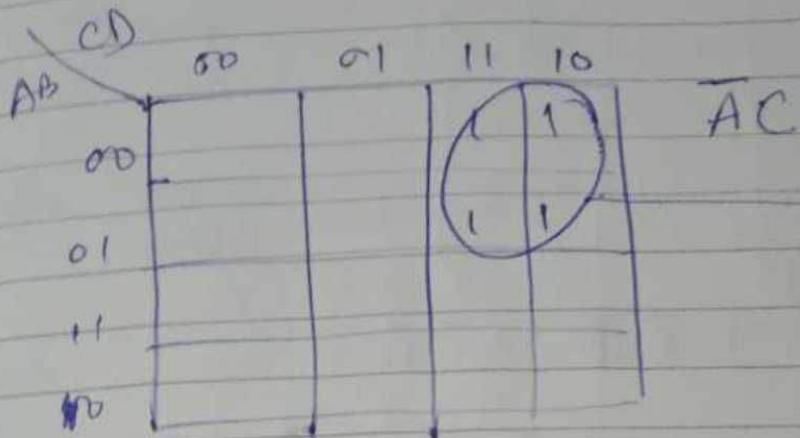


no need to take
double grouping

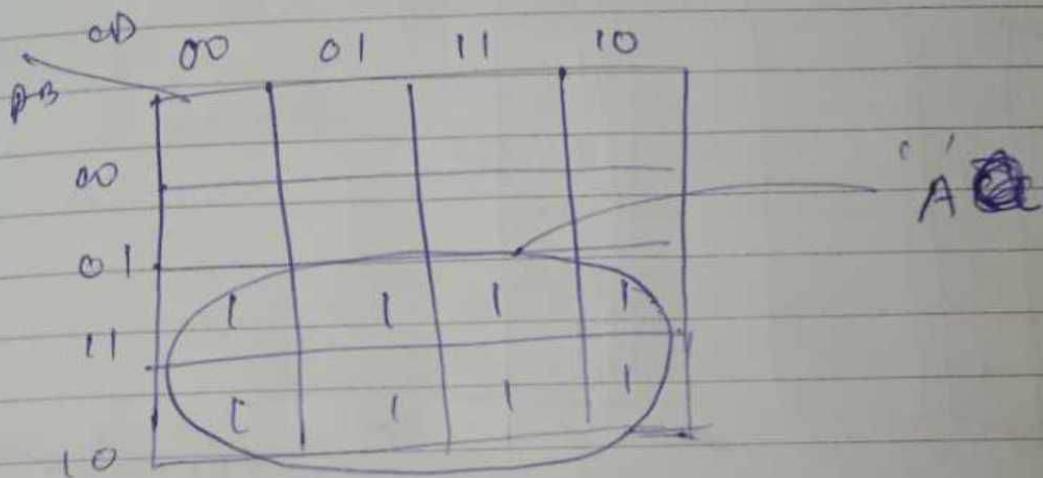


WEDNESDAY • JULY

5	10	11	12	13	14
16	17	18	19	20	21
23	24	25	26	27	28

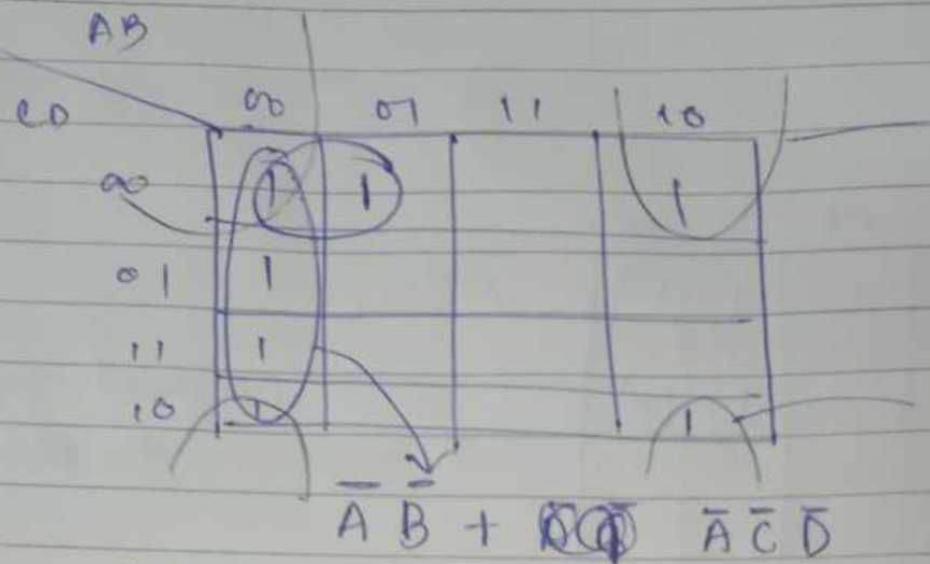

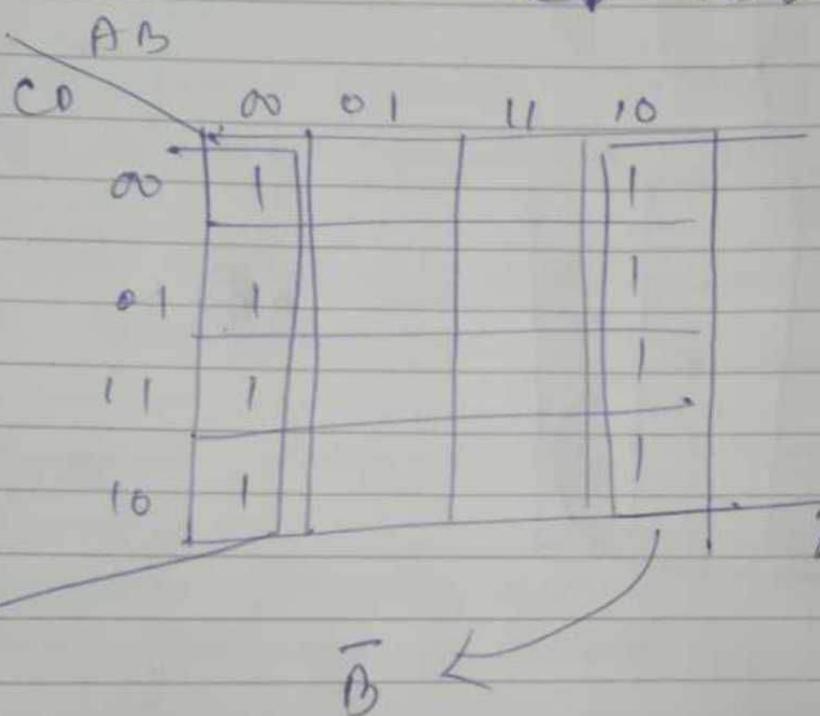see first
if estate
is poss
then
greater
then



14 15 16 17 18
21 22 23 24 25
28 29 30 31

JULY - MONDAY

In the sum of product function $f(x,y,z)$

$$f(x,y,z) = \Sigma(2, 3, 4, 5)$$

The prime implicants are

(a) $\bar{x}y, x\bar{y}$

(gate 2007)

(b) $\bar{x}y, x\bar{y}\bar{z}, x\bar{y}z$


(c) $\bar{x}y\bar{z}, \bar{x}yz, x\bar{y}$

(d) $\bar{x}y\bar{z}, \bar{x}yz, x\bar{y}\bar{z}, x\bar{y}z$.

K-Map Simplification :-

① Two-variable :-

Decimal	A	B
0	0	0
1	1	0
2	0	1
3	1	1

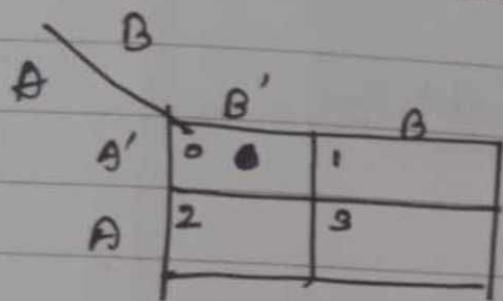

② Three-variable :-

A	BC	$\bar{B}\bar{C}$	$B\bar{C}$	$\bar{B}C$	BC'
0	00	01	11	10	00
1	01	13	2	4	5

A	BC	$\bar{B}\bar{C}$	$B\bar{C}$	$\bar{B}C$	BC'
0	00	01	11	10	00
1	01	13	2	4	5

D	A	B	C
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1

③ Four variable K-Map :-


		CD				
		AB	00	01	11	10
↓	00	0	1	2	3	
	01	4	5	7	6	
	11	12	13	15	14	
	10	8	9	11	10	

① Example for 2-variable :-

$$f = \Sigma (0, 2)$$

OR

$$f = A'B' + AB'$$

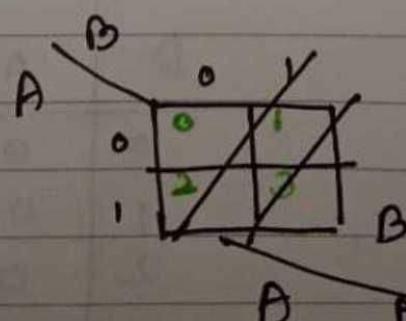

0	0	1	
0	1	0	0
1	0	1	0


Ans:- $f = B'$

S	T	W	T	F	S	S
1	2	3	4	5	6	7
8	9	10	11	12	13	14
15	16	17	18	19	20	21
22	23	24	25	26	27	28
29	30	31				

JULY • SATURDAY

20
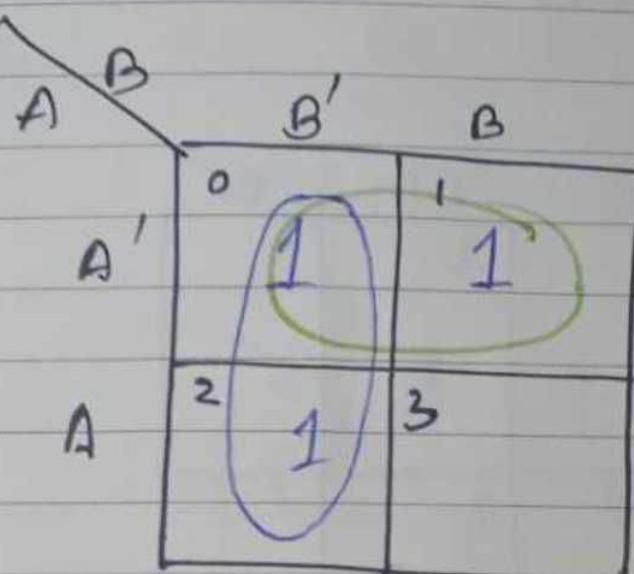
$$\textcircled{2} \quad f = \Sigma(0, 1, 2)$$



$$f = B' + A'$$

WK-29

SUNDAY

2

Example for 3-variable:-

$$\textcircled{1} \quad f = A'B'C' + AB'C'$$

		B'C'	B'C	BC	BC'
		0	1	2	3
A'		1	0	0	0
A	4	1	0	0	0
	A	1	0	0	0

$$f = B'C'$$

AUGUST 2019

	W	T	F	S	S
1		2	3	4	
2		8	9	10	11
3	1	15	16	17	18
4		22	23	24	25
5		28	29	30	31

2019

JULY • TUESDAY

$$\textcircled{2} \quad f(A, B, C) = \sum (0, 2, 4, 5, 6)$$

\overrightarrow{BC}

	$B'C'$	$B'C$	BC	BC'
A'	0 1	1 0	2 0	3 1
A	4 1	5 1	7 0	6 1

$$f = AB' + C'$$

24

WEDNESDAY • JULY

9	10	11	12	13	14	15
16	17	18	19	20	21	22
23	24	25	26	27	28	29

③

~~for A'B'D~~

$$f = A'B'C'D + ABC'D + A'BCD + ABCD \\ + A'B'C'D'$$

24

WEDNESDAY • JULY

S	M	T	W	T	F	S
30						
1	2	3	4	5	6	7
8	9	10	11	12	13	14
15	16	17	18	19	20	21
22	23	24	25	26	27	28
29						

(3) ~~for A'B'D'~~

$$f = A'B'C'D + ABC'D + A'BCD + ABCD \\ + A'B'C'D'.$$

AB	A'B'	A'B	AB	AB'
CD	1	0	0	0
C'D'	0	1	1	0
C'D	0	1	1	0
CD	0	1	1	0
CD'	0	0	0	0

$$f = A'B'C'D + BD$$

N
 1 2 3 4
 8 9 10 11
 7 15 16 17 18
 14 22 23 24 25
 21 29 30 31

JULY • SATURDAY

21

K-map simplification for POS form:-

POS \rightarrow Maxterm

$$\begin{array}{l} 0 \rightarrow A \\ 1 \rightarrow A' \end{array}$$

Minterm

$$\begin{array}{l} 0 \rightarrow A' \\ 1 \rightarrow A \end{array}$$

Two variable

		B	B'
		0	1
A	0	0	1
	1	2	3

D	A	B	MaxTerm
0	0	0	$A + B$
1	0	1	$A + B'$
2	1	0	$A' + B$
3	1	1	$A' + B'$

		B	B'
		$A + B$	$A + B'$
A	0	$A + B$	$A + B'$
	1	$A' + B$	$A' + B'$

WK 30 (209-156)

28

SUNDAY

AUGUST

29

MONDAY • JULY

④ Three variable

		$B+C$	$B+C'$	$B'+C$	$B'+C'$
		0	1	3	2
		4	5	7	6
A					
A'					

⑤ Similarly for four variable . . . same pr

B. $f = (A + B + C') (A + B' + C') (A + B + C)$


		$B+C$	$B+C'$	$B'+C$	$B'+C'$
		0	0	0	
A					
A'					

$$f = (A + B) (A + C')$$

K-Map (Don't Care Condition)

① $f(A, B, C, D) = \sum m(0, 2, 3, 6, 7, 12, 13, 14)$
~~SOP~~ + $\sum d(1, 4, 11, 15)$

↑
 don't care cond.

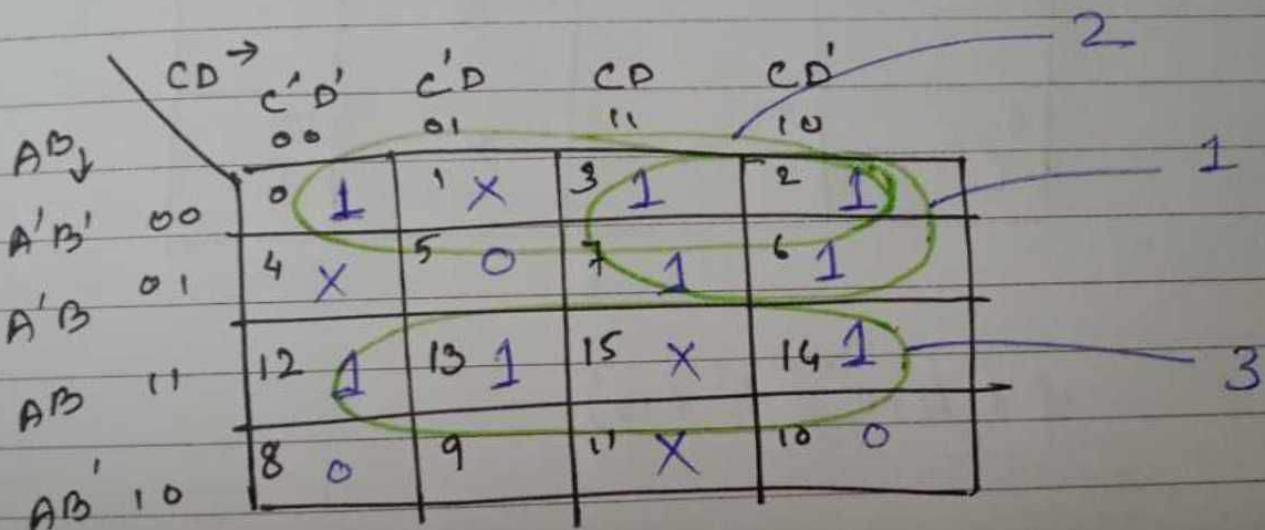


$$f = A'B' + CA' + AB$$

10

SATURDAY • AUGUST

1	2	3	4
7	8	9	10
14	15	16	17
21	22	23	24
28	29	30	31
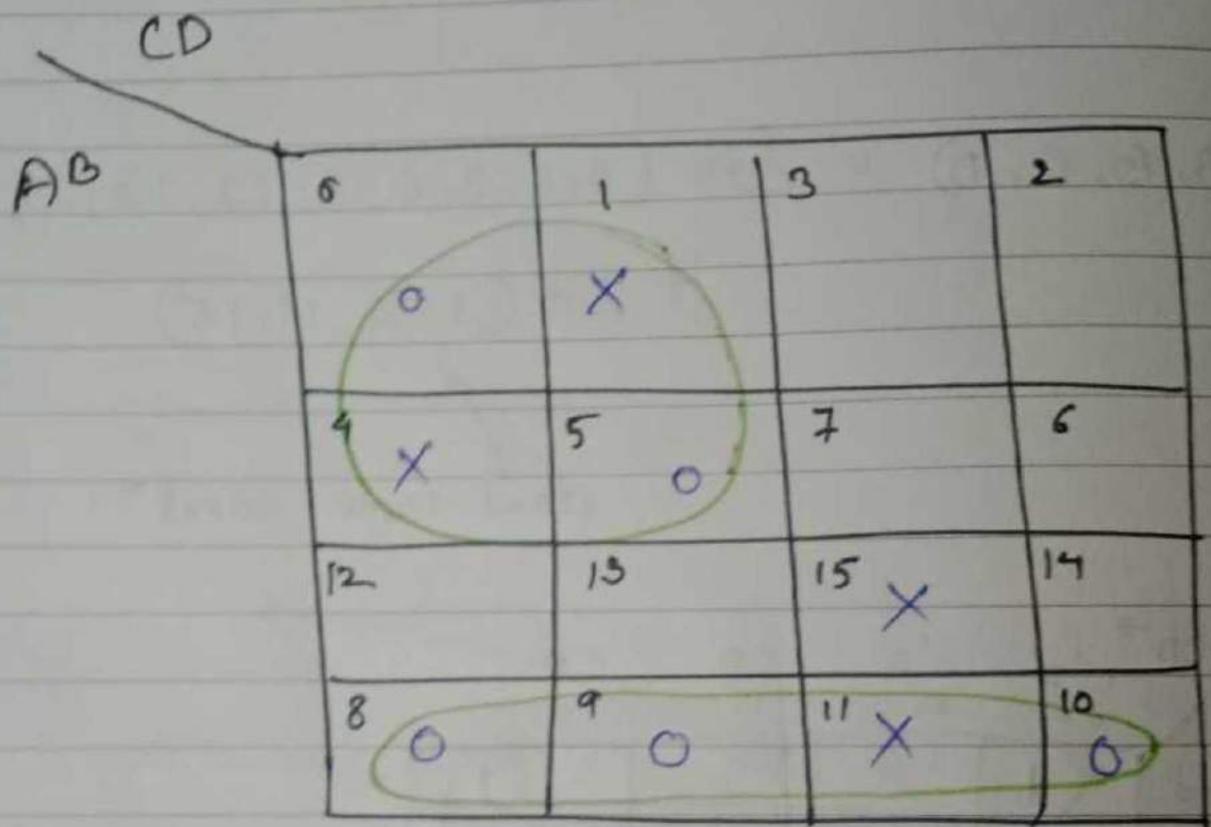
$$② f(A, B, C, D) = \pi M(5, 8, 9, 10) \pi D(1, 4, 11, 15)$$



$$f = (A + c)(A' + B)$$

9 10 11 12 13 14
15 16 17 18 19 20 21 22
23 24 25 26 27 28 29

AUGUST • MONDAY

1 2

Questions

- ① Reduce using mapping the expression

$$f = \Sigma m (2, 3, 6, 7, 8, 10, 11, 13, 14)$$

- ② Reduce the following expression to the simplest possible POS & SOP forms


$$f = \Sigma m (6, 9, 13, 18, 19, 25, 27, 29, 31)$$

$$+ d (2, 3, 11, 15, 17, 24, 28)$$

COMBINATIONAL CIRCUITS

28 29 30 24 25 26

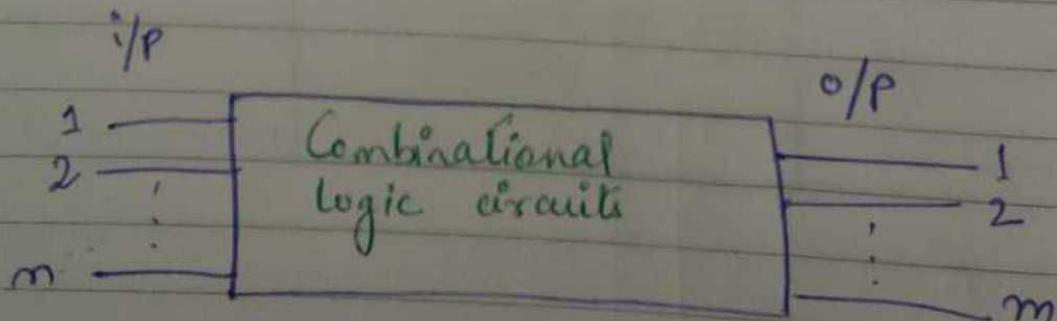- 9 ↳ output is dependent upon combination of input variables.
 - 10
 - 11 ↳ Does not use any memory.
 - 12 ↳ It can have '~~n~~' 'n' no. of inputs & 'm' no. of outputs.
 - 13 ↳ eg:- Adders & Subtractors
Decoders
Comparators
MUX
Code Converters
ROM
PLA
PAL



COMPARISON BETWEEN CKTSCOMBINATIONAL & SEQUENTIALCombinational

↳ O/P is dependent on the present input

↳ ex- Adder


$$\begin{array}{r} 1 \\ + 0 \\ \hline 1 \end{array}$$

↳ O/P depends on the present i/p as well as previous O/P or O/Ps.

↳ Counter (ex)

+1 to the previous O/P

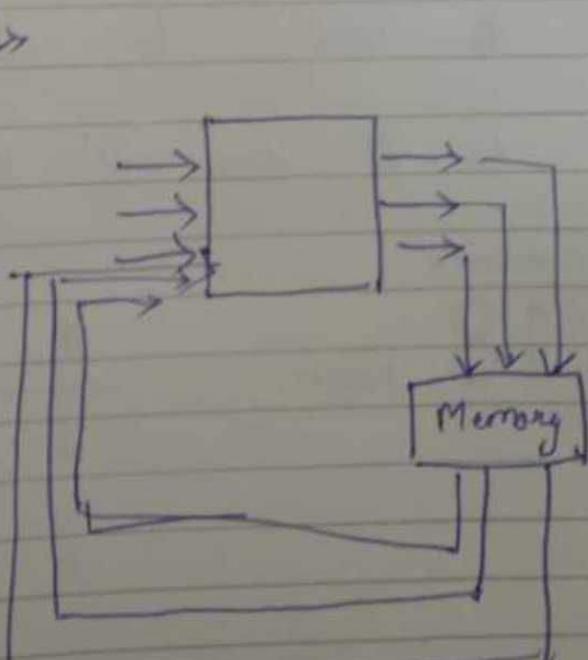If O/P is 5 that means previous O/P was 4 to which 1 is added



(+) Feedback.

17

SATURDAY • AUGUST

S	M	T	W	T	F	S
1	2	3	4	5	6	7
8	9	10	11	12	13	14
15	16	17	18	19	20	21
22	23	24	25	26	27	28
29	30	31				

HALF ADDER

$$S = A \oplus B$$

$$C_0 = A \cdot B$$

→ used to add a single bit nos.


→ It does not take carry from previous sum.

18

SUNDAY


A	B	S	C ₀	
0	0	0	0	Binary Addition
0	1	1	0	
1	0	1	0	
1	1	0	1	
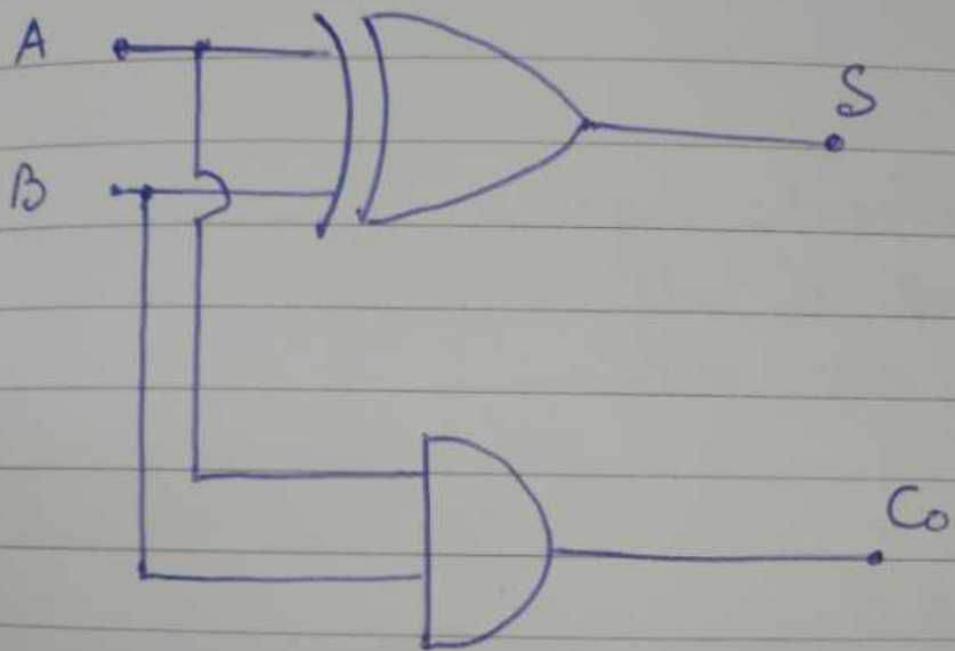
$$\boxed{S = A \oplus B}$$
$$C_0 = A \cdot B$$



20

TUESDAY • AUGUST

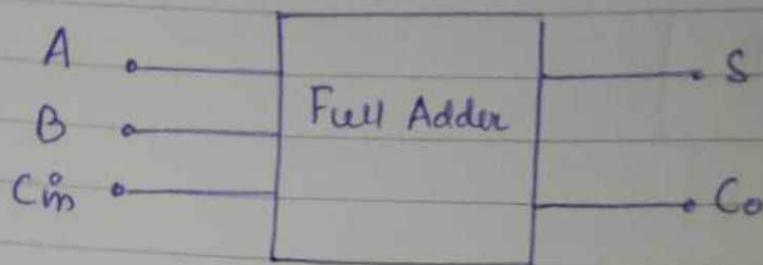FULL ADDER :-

Full Adder is a arithmetic logic circuit designed to add two single bit nos. with a carry.

$$\begin{array}{r}
 & A & 0 & 0 \\
 & B & 0 & 1 \\
 & C & 0 & 1 \\
 \hline
 & & & 0
 \end{array}$$

T.T.

A	B	Cin	S	Co
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	1	1
1	1	1	0	1

Sum

		00	01	11	10
		0	1	0	1
		1	1	0	0
A	BCin				

Checkboard configuration



$$S = A \oplus B \oplus C_{in}$$

Carry out

		00	01	11	10
		0	0	1	0
		1	0	1	1
A	BCin				

$$C_0 = BC_{in} + AB + AC_{in}$$

$$= AB + BC_{in} + C_{in}A$$

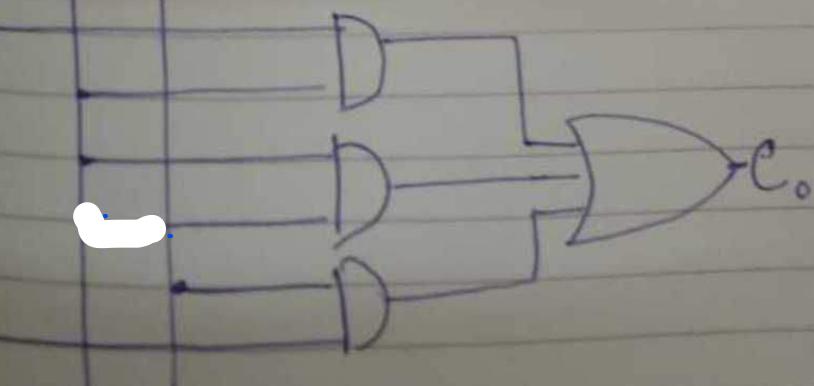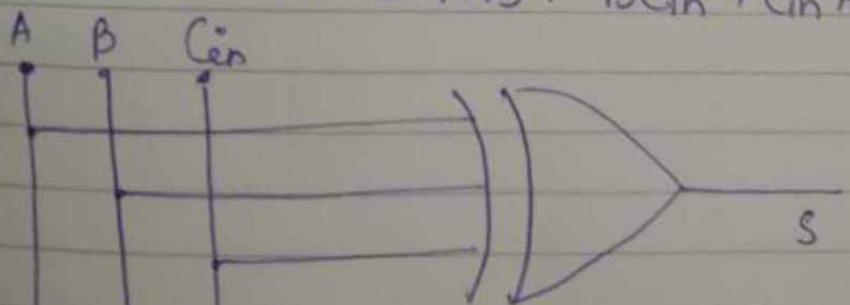

31


SATURDAY • AUGUST

1	16	2	17
7	1	2	4
14	15	16	18
21	22	23	24
28	29	30	31

COMBINATIONAL CIRCUITS

Full Adder using Half adder:-

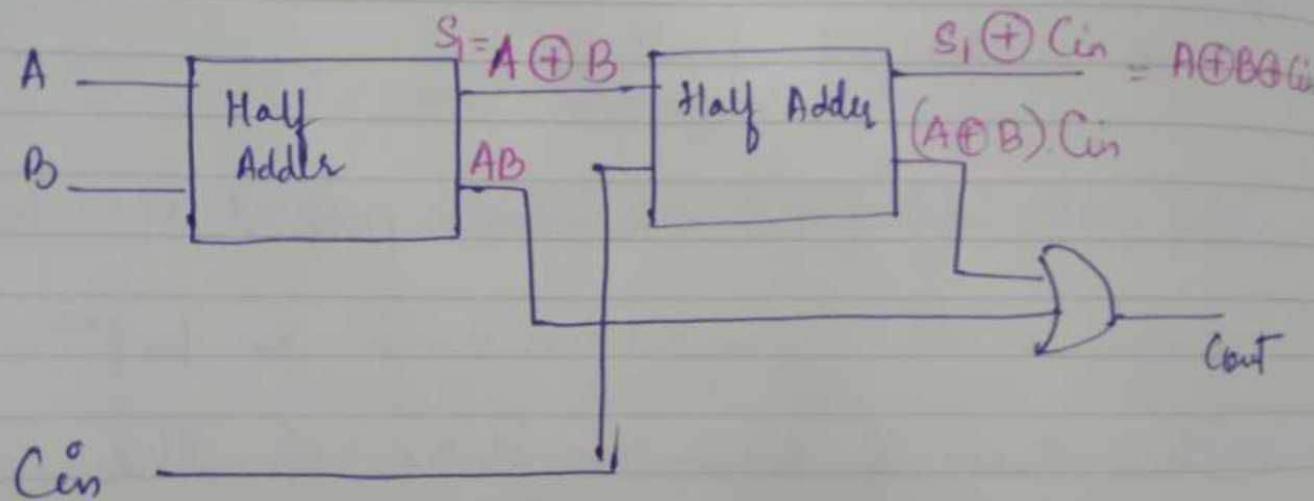- * If full adder not available & we have only half adders, we can design full adder using two half adders.




Half Adder $S_1 = A \oplus B$
 $C_{arry} = A \cdot B$

$$C_{out} = (A \oplus B) C_{in} + AB$$

$$\begin{aligned} A + \bar{A}B \\ = A + B \end{aligned}$$

COMBINATIONAL CIRCUITS.Full Adder using Half Adder :-

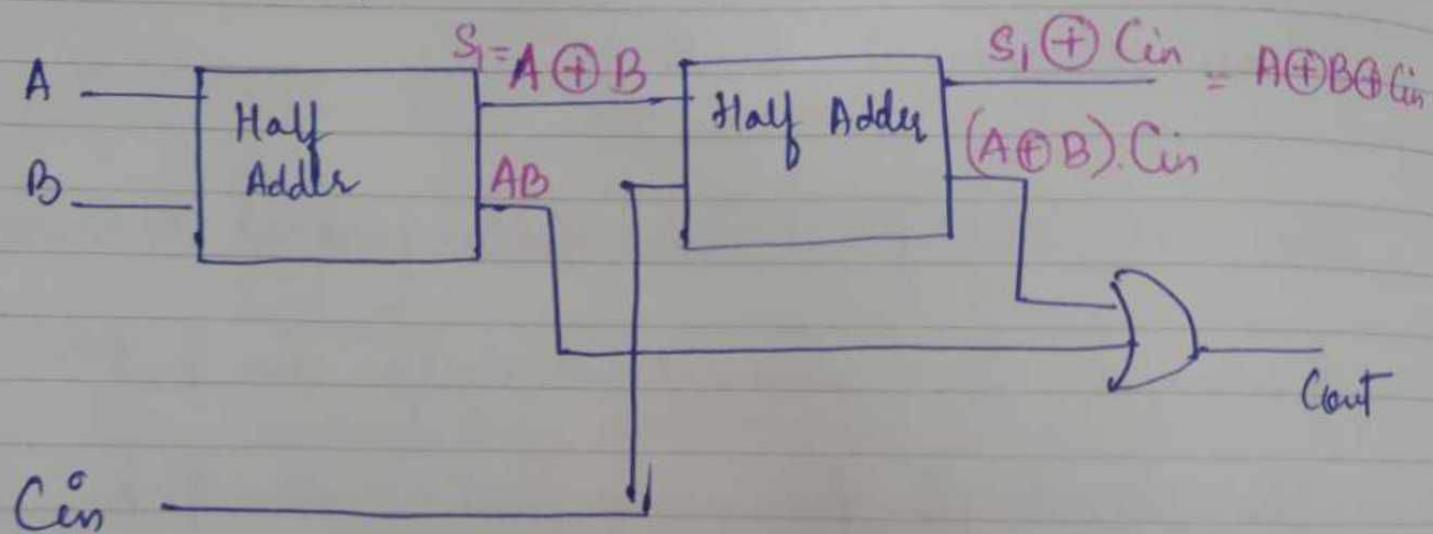* If full adder not available & we have only half adders, we can design full adder using two half adders.



Half Adder $S_1 = A \oplus B$
 $\text{Carry} = A \cdot B.$

$$\begin{aligned}
 \text{Cout} &= (A \oplus B) \text{Cin} + AB \\
 &= (\bar{A}B + A\bar{B}) \text{Cin} + AB \\
 &= \bar{A}B \text{Cin} + A\bar{B} \text{Cin} + AB \\
 &= B(\bar{A}\text{Cin} + A) + A\bar{B}\text{Cin} \\
 &= B(A + \text{Cin}) + \bar{B}A\text{Cin}
 \end{aligned}$$

$$\begin{aligned}
 A + \bar{A}B \\
 = A + B
 \end{aligned}$$

(244-121) WK 35

01

SUNDAY • SEPTEMBER

2019			
5	16	17	18
4	5	6	7
11	12	13	14
18	19	20	21
25	26	27	28

$$= AB + BC_{in} + \bar{B}AC_{in}$$

$$= AB + BC_{in} + (B + \bar{B}A)C_{in}$$

$$= AB + (A + B)C_{in}$$

$$= AB + BC_{in} + C_{in}A$$

Self study


Subtractors

N Bit parallel Adder :-

↳ cascade of full adder

↳ device for adding multi bit nos.

4-bit Parallel Adder :-

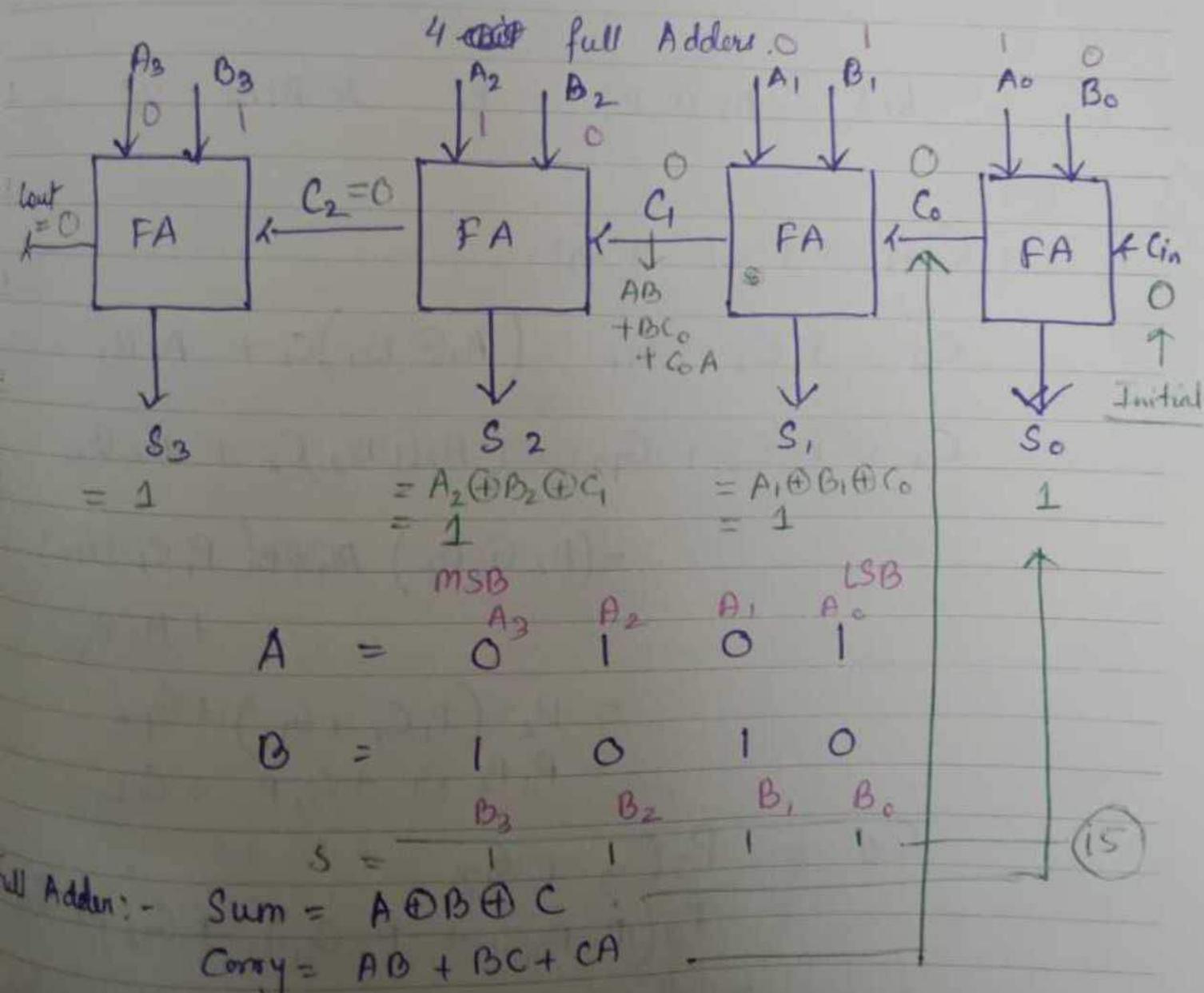


07

SATURDAY • SEPTEMBER

4	5	6	7	8	9
11	12	13	14	15	16
18	19	20	21	22	23
25	26	27	28	29	30

DECODERS

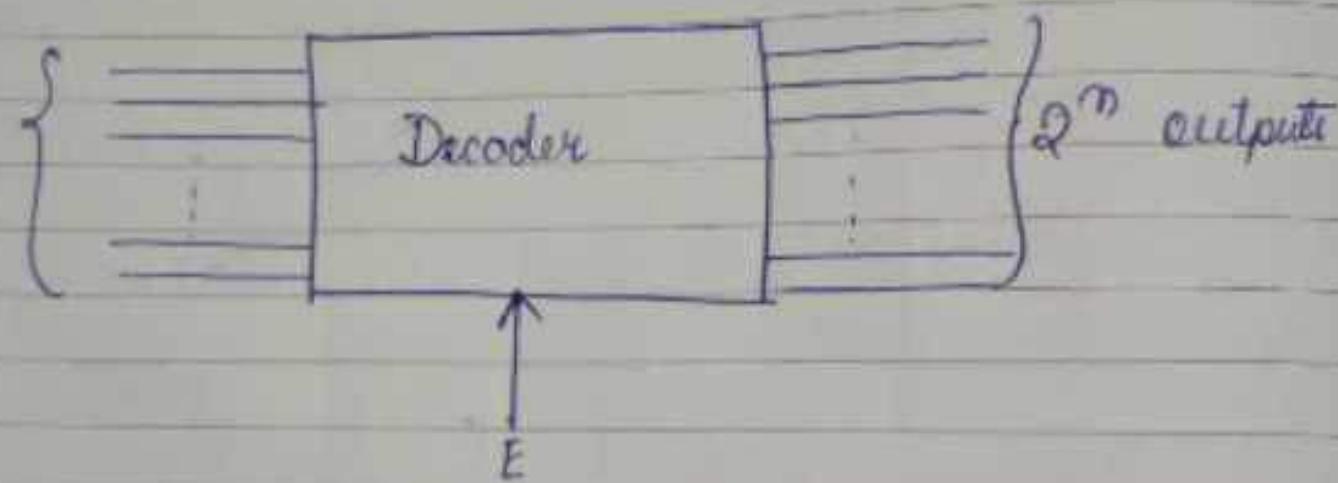- * Decoder is a multi-input, multi-output logic circuit which decodes 'm' inputs into 2^n possible outputs.



where $E = \text{enable}$

- $E = 0$, decoder is disabled.
(OFF)
- $E = 1$, Decoder is enabled.
(ON)

If 2 inputs are provided
we will get 2^n o/p

2 3 4 5 6
 9 10 11 12 13
 16 17 18 19 20
 23 24 25 26 27
 30 31

SEPTEMBER • MONDAY

09

2 to 4 Decoder Design :-

2 i/p , 4 o/p

$n=3 \rightarrow 2^3$
 $n=2 \rightarrow 2^2$
 $n=1 \rightarrow 2^1$
 $n=0 \rightarrow 2^0$

E	A	B	y_3	y_2	y_1	y_0
---	---	---	-------	-------	-------	-------

0	X	X	0	0	0	0
---	---	---	---	---	---	---

1	0	0	0	0	0	1
---	---	---	---	---	---	---

1	0	1	0	0	1	0
---	---	---	---	---	---	---

1	1	0	0	1	0	0
---	---	---	---	---	---	---

1	1	1	1	0	0	0
---	---	---	---	---	---	---

If E=0, without knowing i/p, o/p's are '0'.

when $n=0$, 2^0 is enabled

when $n=1$, 2^1 place enabled

so - on


$$y_3 = A \cdot B$$

$$y_2 = A \cdot \bar{B} \quad (\text{see the table})$$

$$y_1 = \bar{A} \cdot B$$

$$y_0 = \bar{A} \cdot \bar{B}$$

Logic Diagram :-

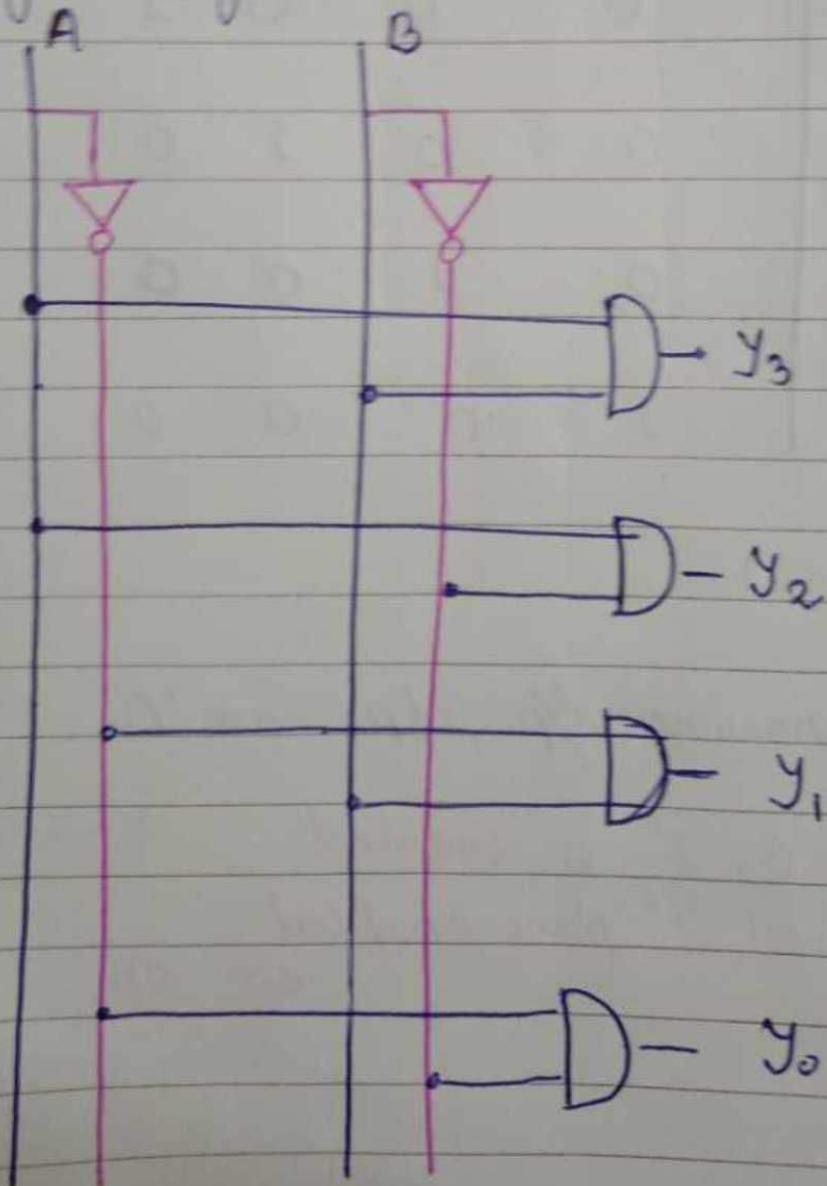


3 to 8 Decoder (self study)

$$n=3, 2^3 = 8 \text{ o/p's}$$

MULTIPLEXER (MUX)

↳ Multiplexer is a combinational logic circuit used to select only one o/p output among several inputs based on selection lines.

↳ This can act as digital switch.

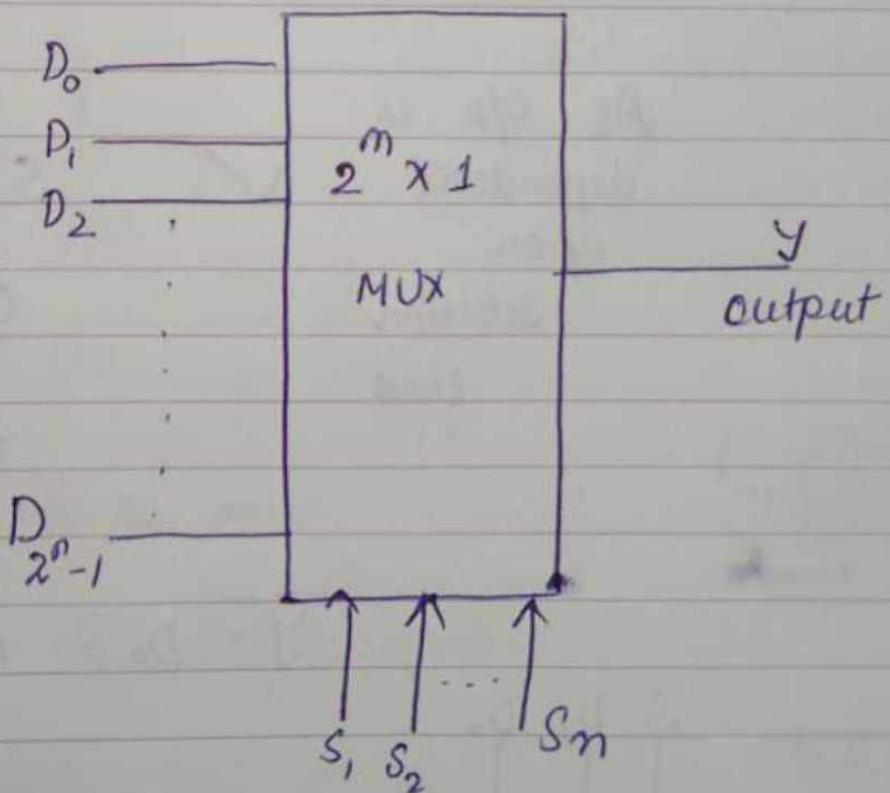

↳ This is also called as data selector.


↳ For a MUX, there can be 2^n i/p's, 'n' selections lines

and only one o/p.

12

THURSDAY • SEPTEMBER

SUN	MON	TUE	WED	THU	FRI	SAT
1	2	3	4	5	6	7
8	9	10	11	12	13	14
15	16	17	18	19	20	21
22	23	24	25	26	27	28

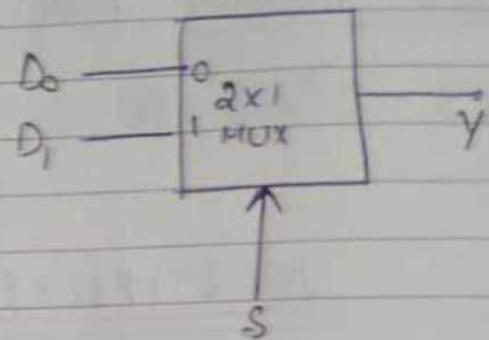2 x 1 MUX Design :-jj

D ₀	D ₁	S	Y
----------------	----------------	---	---

X

As O/P is

dependent

upon

selection

line

✓

S

Y

0

D₀

1


D₁S D₁ D₀

$$Y = D_0 \bar{S} + D_1 S$$

4×1 MUX :-

$$2^n = 4$$

$$\therefore n = 2$$

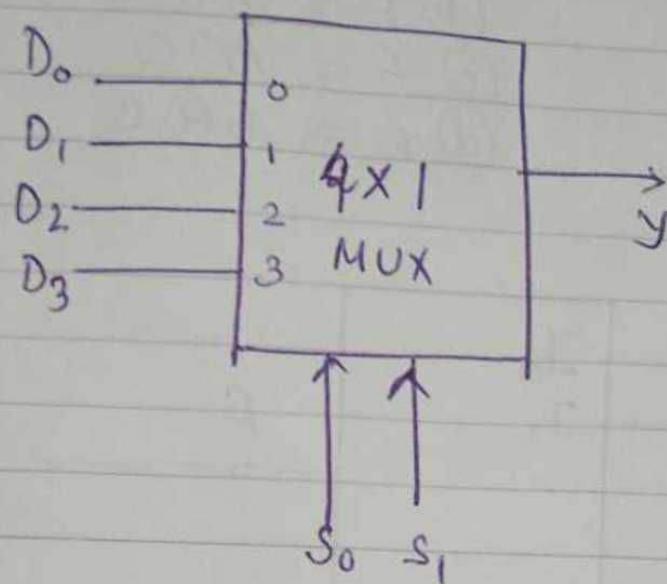

S_0	S_1	y
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3

$$y = D_0 \bar{S}_0 \bar{S}_1 + D_1 \bar{S}_0 S_1 + D_2 S_0 \bar{S}_1 + D_3 S_0 S_1$$

Logic Diagram \rightarrow ?

14



SATURDAY • SEPTEMBER

2019 AUGUST

S	M	T	W	T	F	S
4	5	6	7	8	9	10
11	12	13	14	15	16	17
18	19	20	21	22	23	24
25	26	27	28	29	30	31

Q1 The logic realized by the circuit shown in the figure is -

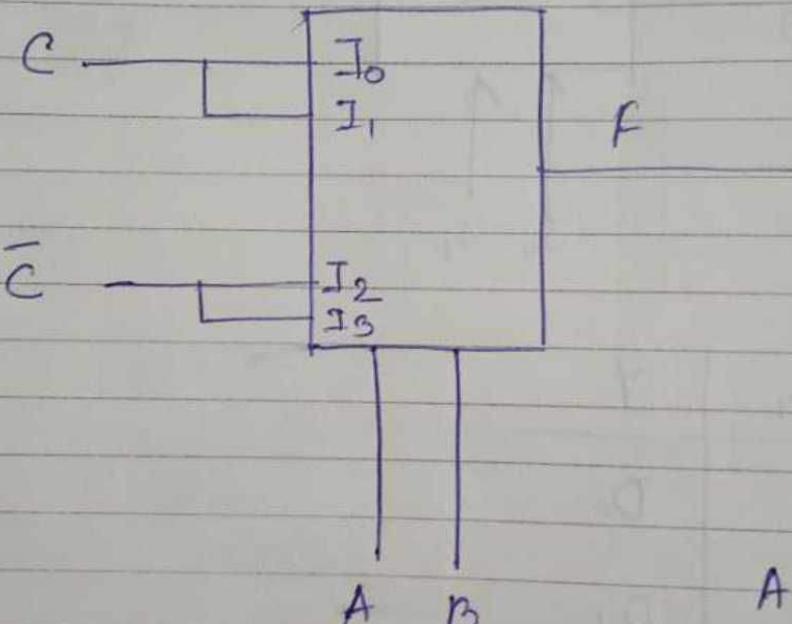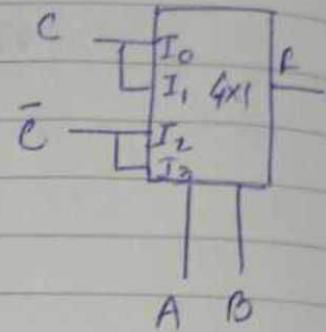- (a) $F = A \odot C$
- (b) $F = A \oplus C$
- (c) $F = B \odot C$
- (d) $F = B \oplus C$



A	B	F
0	0	C
0	1	C
1	0	\bar{C}
1	1	\bar{C}

15

SUNDAY



$$\begin{aligned}
 F &= C\bar{A}\bar{B} + C\bar{A}B + \bar{C}A\bar{B} + \bar{C}AB \\
 &= C\cancel{\bar{A}}(C\bar{A}) + \bar{C}A \\
 &= A \oplus B
 \end{aligned}$$

M	T	W	T	F	S	S
1	2	3	4	5	6	
8	9	10	11	12	13	
15	16	17	18	19	20	
22	23	24	25	26	27	
29	30	31				

SEPTEMBER • MONDAY

16

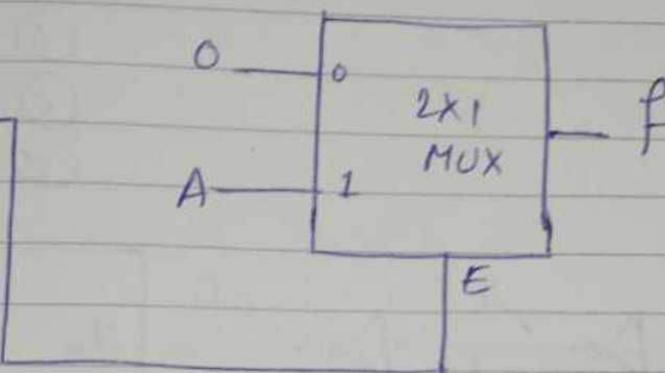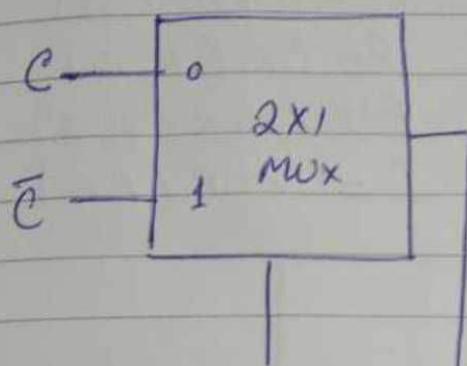Q2. The Boolean 'f' implemented in the figure using two input multiplexers is



B

(a) $A\bar{B}C + A\bar{B}\bar{C}$

(b) $ABC + A\bar{B}\bar{C}$

(c) $\bar{A}BC + \bar{A}\bar{B}\bar{C}$

(d) $\bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C}$

1st MUX

B	E
0	C
1	\bar{C}

$$E = C\bar{B} + \bar{C}B$$

2nd MUX

E	f
0	0
1	A


$$\begin{aligned} f &= AE \\ &= A(C\bar{B} + \bar{C}B) \\ &= A\bar{B}C + A\bar{C}\bar{B} \end{aligned}$$

TUESDAY • SEPTEMBER

11	12	13	14	15	16
18	19	20	21	22	23
25	26	27	28	29	30

Q3. The logic function implemented by the circuit below is —

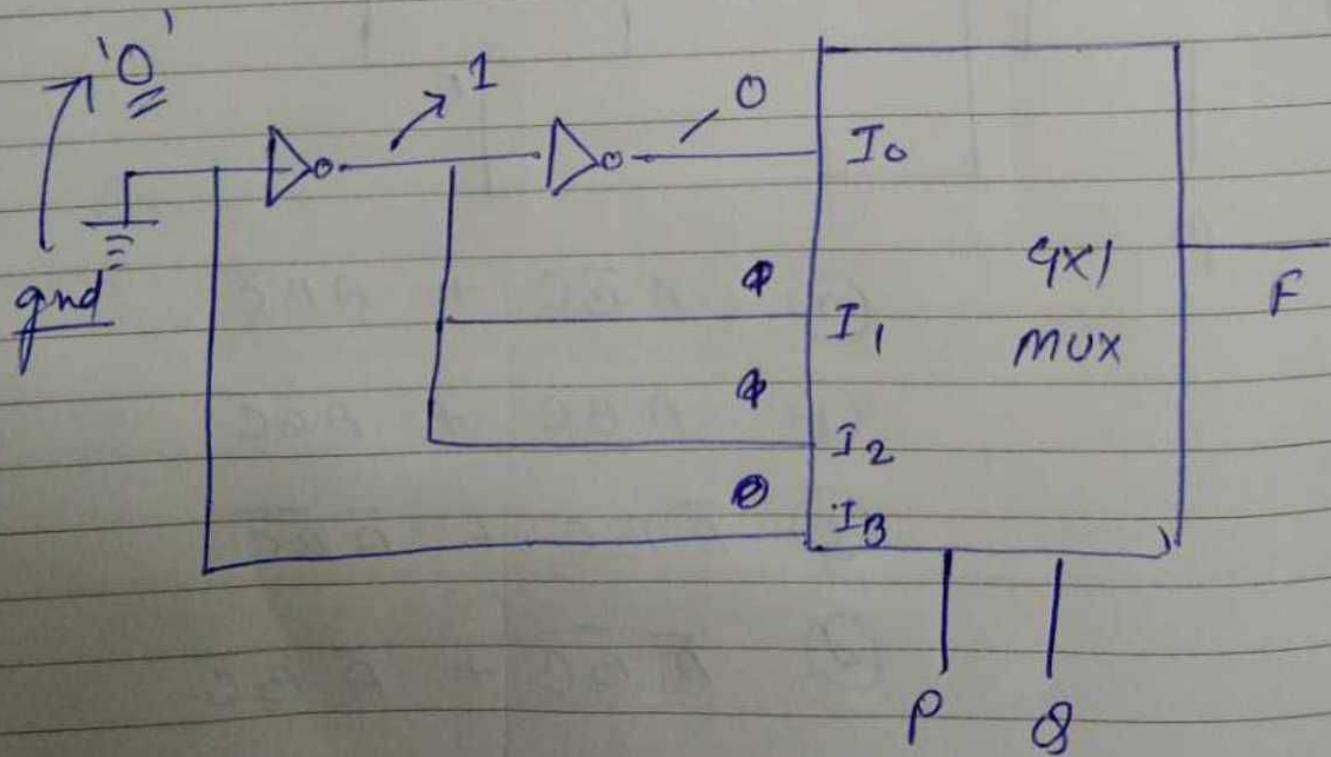- (a) $F = \text{AND}(P, Q)$
- (b) $P = \text{OR}(P, Q)$
- (c) $F = \text{XNOR}(P, Q)$
- (d) $F = \text{XOR}(P, Q)$



October						
M	T	W	T	F	S	S
1	2	3	4	5	6	7
8	9	10	11	12	13	14
15	16	17	18	19	20	21
22	23	24	25	26	27	28
29	30	31				


SEPTEMBER • WEDNESDAY

18

DEMULTIPLEXERS (DEMUX)

- 8 ↳ one I/P and many O/Ps.
- 9 ↳ Reverse operation of MUX.
- 10 ↳ Also called as Data Distributor.
- 11 ↳ Demux is a combinational ckt.

MUX	Demux
2:1 / 2x1	1:2 / 2x1
8:1 / 8x1	⊗ 1:8
4:1	⊗ 1:4

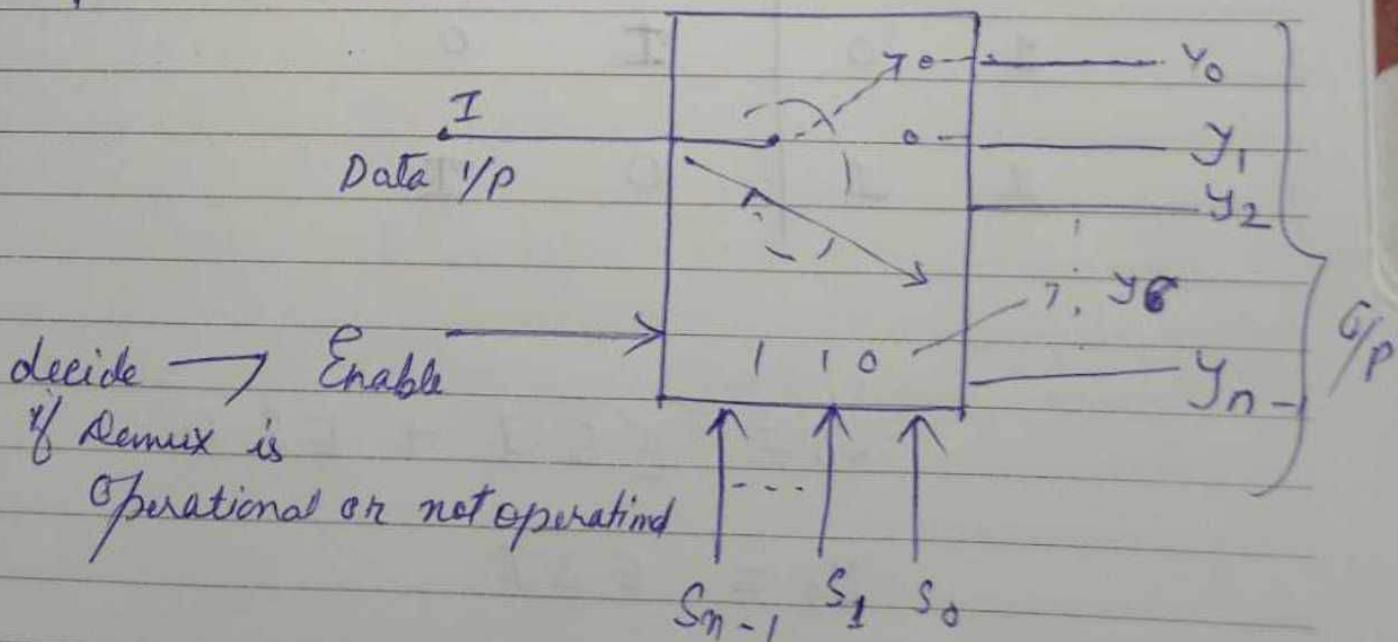

Select line '110' then (c) the data I/P will go to Y₀.

OCTOBER


NOVEMBER

19

THURSDAY • SEPTEMBER

4	5	6	7
11	12	13	14
18	19	20	21
25	26	27	28

1 : 2 Demux

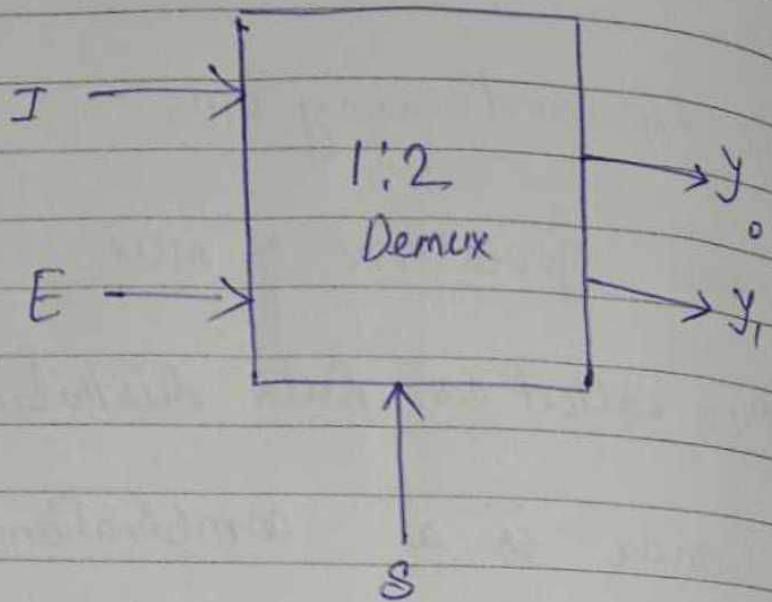

E	S	y ₀	y ₁
0	0	0	0
0	1	0	0
1	0	1	0
1	1	0	1

$$y_0 = \bar{E} \bar{S} \cdot I + E S \cdot 0$$

$$y_0 = \bar{E} \bar{S} I$$


$$y_1 = E S I$$

8 9 10 11 12 13
14 15 16 17 18 19 20
21 22 23 24 25 26 27
28 29 30 31

SEPTEMBER • FRIDAY

20

logic Diagram

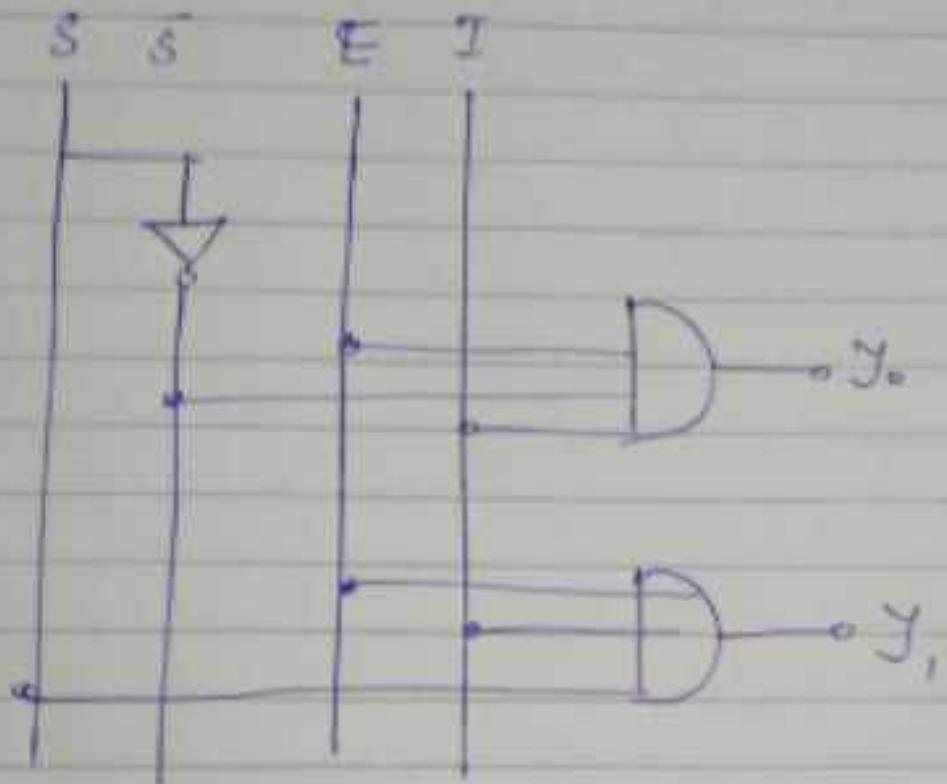

26/09


Q. Implement the following fn using a MUX:-
 $F(A, B, C) = \Sigma m(1, 3, 5, 6)$

Sol^m:

	A	B	C		F
0	0	0	0		0
1	0	0	1		1
2	0	1	0		0
3	0	1	1		1
4	1	0	0		0
5	1	0	1		1
6	1	1	0		1
7	1	1	1		0

26-100) WK 38
22

SUNDAY

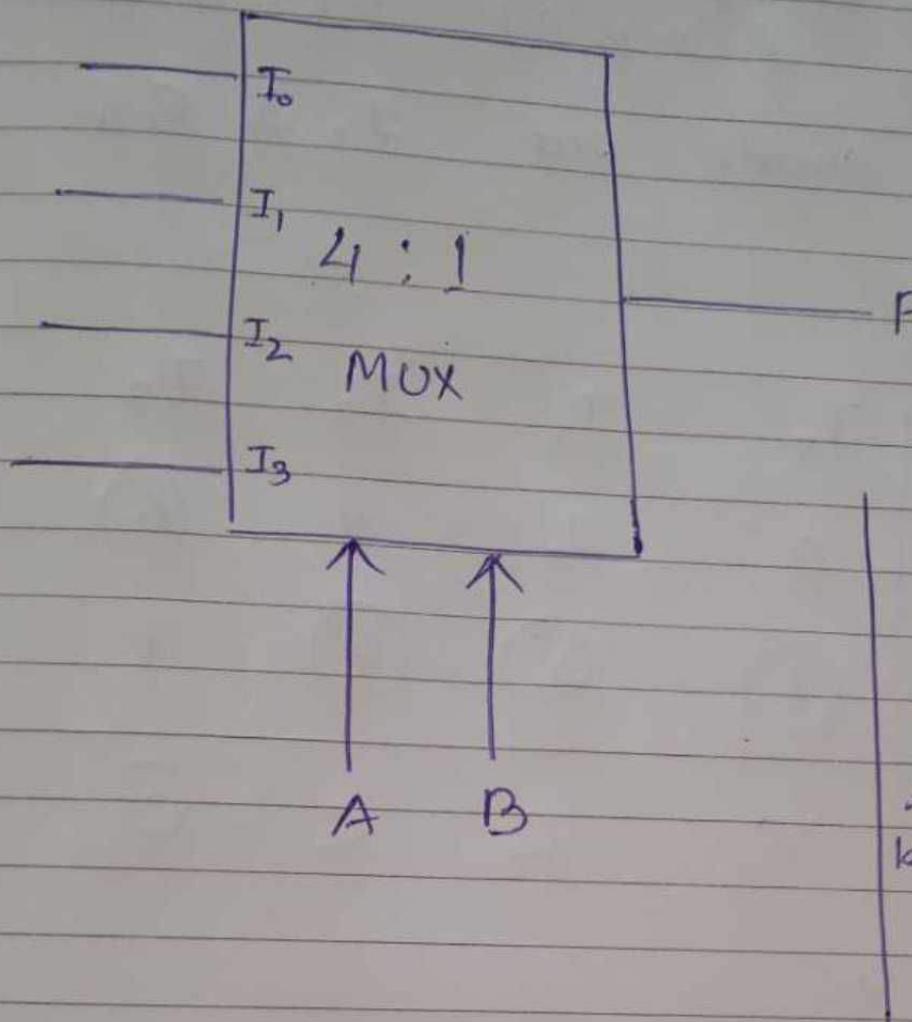

A	B	F
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

	I_0	I_1	I_2	I_3
\bar{C}	0	0	4	6
C	1	3	5	7

see where
value of C = 0

$C=1$

24

TUESDAY • SEPTEMBER

Now see the f^n
 $f(A, B, C) = 2(1, 3, 5, 6)$

circle out 1, 3, 5, 6

	T_0	T_1	T_2	T_3
$\bar{0}$	0	2	4	6
c	1	3	5	7

$$\textcircled{O} \quad \textcircled{O} \quad - \quad \times$$

$$\textcircled{O} \quad - \quad \textcircled{O} \quad \times$$


$$\underline{+ \bar{C} \quad C \quad O}$$

OCTOBER - 2019
T W T F S S
1 2 3 4 5 6
7 8 9 10 11 12 13
14 15 16 17 18 19 20
21 22 23 24 25 26 27
28 29 30 31

Wk 39 (268-0987)

SEPTEMBER • WEDNESDAY

25

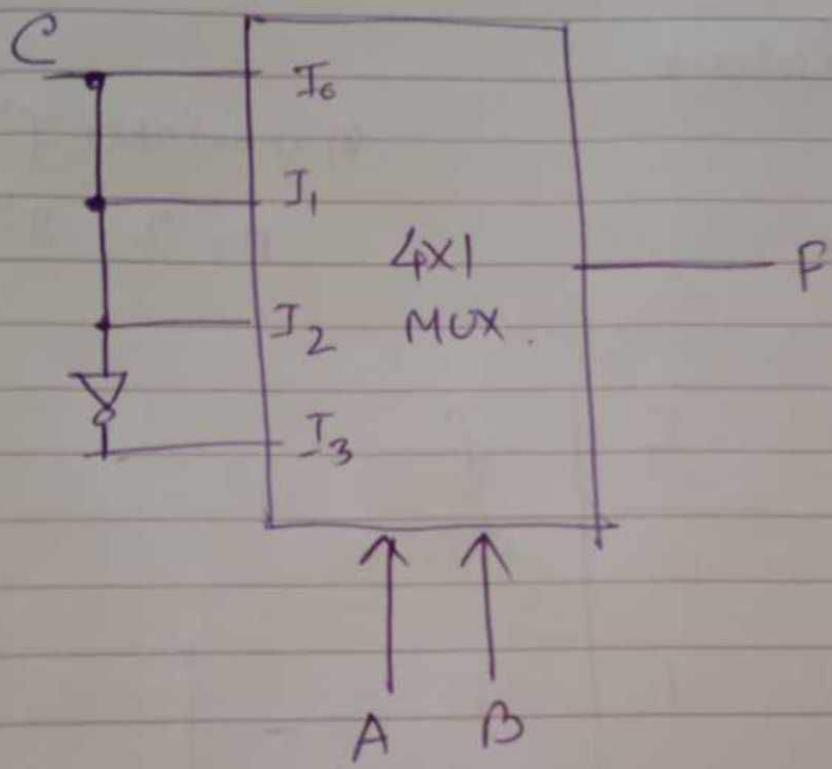

26

2019


THURSDAY • SEPTEMBER

4	5	6	7	8	9	10	11
11	12	13	14	15	16	17	18
18	19	20	21	22	23	24	25
25	26	27	28	29	30	31	32

Q. Implement $f = \Sigma m(1, 2, 3, 6, 7)$ using multiplexer

8X1 MUX

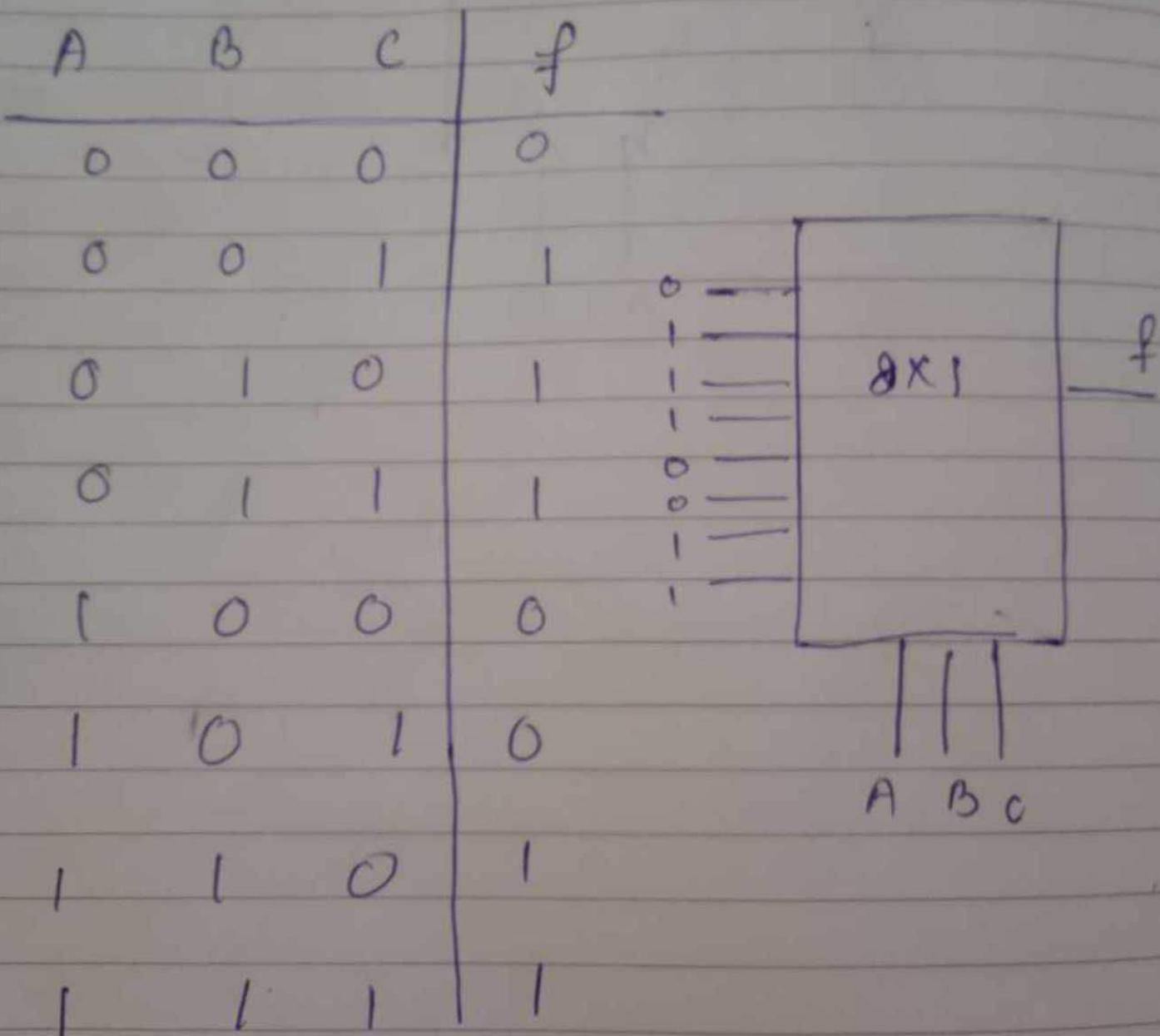if variable f 2^n min terms
 $n = 3, 2^3 = 8 \rightarrow 0-7$



4x1 MUX

A	B	C	f
0	0	0	0 } 0
0	0	1	1 } C
0	1	0	1 } 1
0	1	1	1 } 1
1	0	0	0 } 0
1	0	1	0 } 1
1	1	0	1 } 1
1	1	1	1 } 1

C ——————
1 ——————
0 ——————
1 ——————
4x1
MUX —————— f
A ||| B

28

SATURDAY • SEPTEMBER

29 30 31 32 33 34 35

31

A	B	C	f
---	---	---	---

0	0	0	0
---	---	---	---

0	0	1	1
---	---	---	---

0	1	0	0
---	---	---	---

0	1	1	1
---	---	---	---

1	0	0	0
---	---	---	---

1	0	1	1
---	---	---	---

1	1	0	1
---	---	---	---



1	1	1	0
---	---	---	---

$0 \} f = c$

$0 \} f = c$

$0 \} f = c$

$0 \} f = \bar{c}$

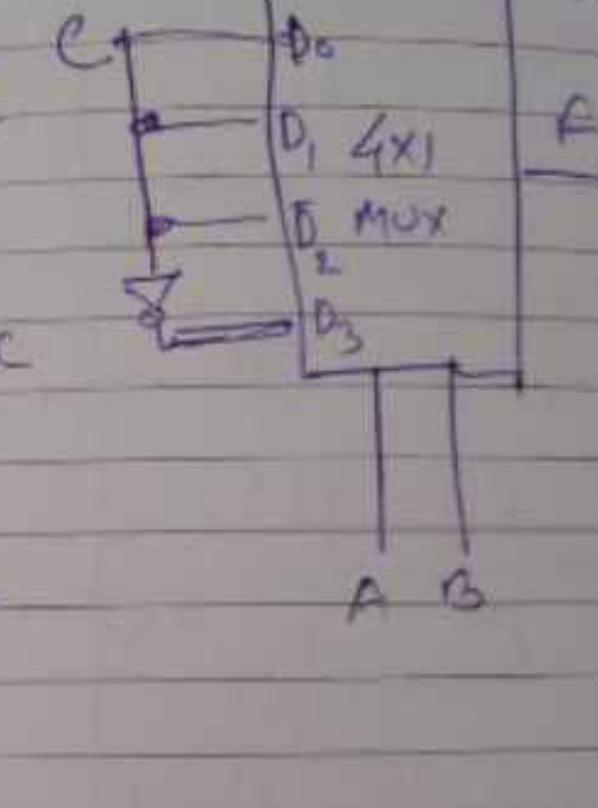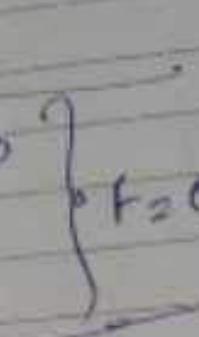

MONDAY

9

SUNDAY