


07

SATURDAY • SEPTEMBER

4	5	6	7	8	9	10
11	12	13	14	15	16	17
18	19	20	21	22	23	24
25	26	27	28	29	30	31

DECODERS

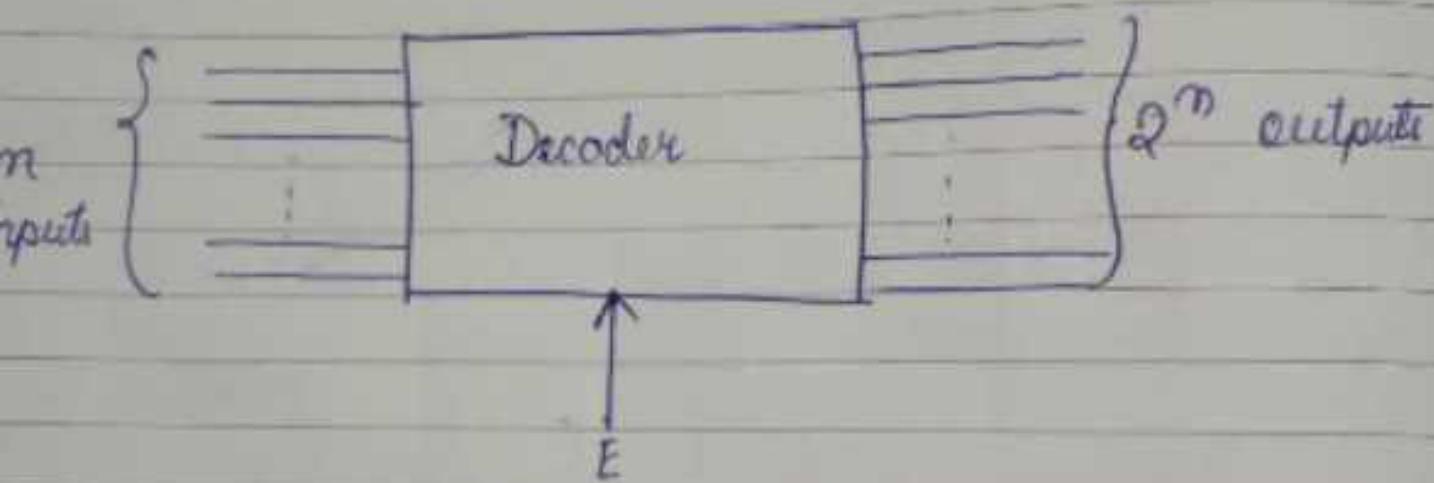- * Decoder is a multi-input, multi-output logic circuit which decodes 'm' inputs into 2^n possible outputs.



where $E = \text{enable}$

- $E=0$, decoder is disabled.
(OFF)
- $E=1$, Decoder is enabled.
(ON)

If 2 inputs are provided
we will get 2^n o/p

8

SUNDAY

2 3 4
 9 10 11 12 13
 16 17 18 19 20
 23 24 25 26 27
 30 31

SEPTEMBER • MONDAY

09

2 to 4 Decoder Design :-

2 i/p , 4 o/p

$n=3 \rightarrow 2^3$
 $n=2 \rightarrow 2^2$
 $n=1 \rightarrow 2^1$
 $n=0 \rightarrow 2^0$

E	A	B	y_3	y_2	y_1	y_0
---	---	---	-------	-------	-------	-------

0	x	x	0	0	0	0
---	---	---	---	---	---	---

1	0	0	0	0	0	1
---	---	---	---	---	---	---

1	0	1	0	0	1	0
---	---	---	---	---	---	---

1	1	0	0	1	0	0
---	---	---	---	---	---	---

1	1	1	1	0	0	0
---	---	---	---	---	---	---

If E=0, without knowing i/p, o/p's are '0'.

when $n=0$, 2^0 is enabled

when $n=1$, 2^1 place enabled

so - on


$$Y_3 = A \cdot B$$

$$Y_2 = A \cdot \bar{B} \quad (\text{see the table})$$

$$Y_1 = \bar{A} \cdot B$$

$$Y_0 = \bar{A} \cdot \bar{B}$$

Logic Diagram :-

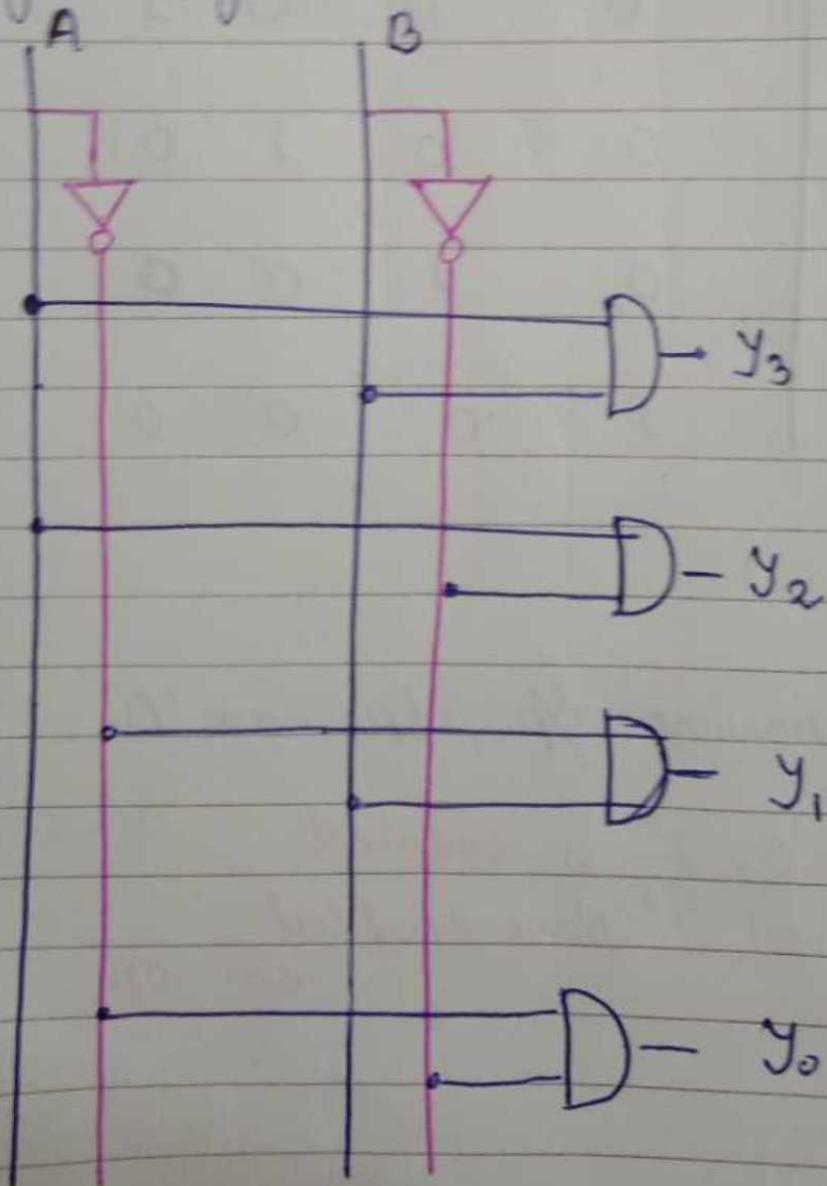

3 to 8 Decoder (self study)

$$n=3, 2^3 = 8 \text{ o/p's}$$


MULTIPLEXER (MUX)

↳ Multiplexer is a combinational logic circuit used to select only one o/p output among several inputs based on selection lines.

↳ This can act as digital switch.


↳ This is also called as data selector.

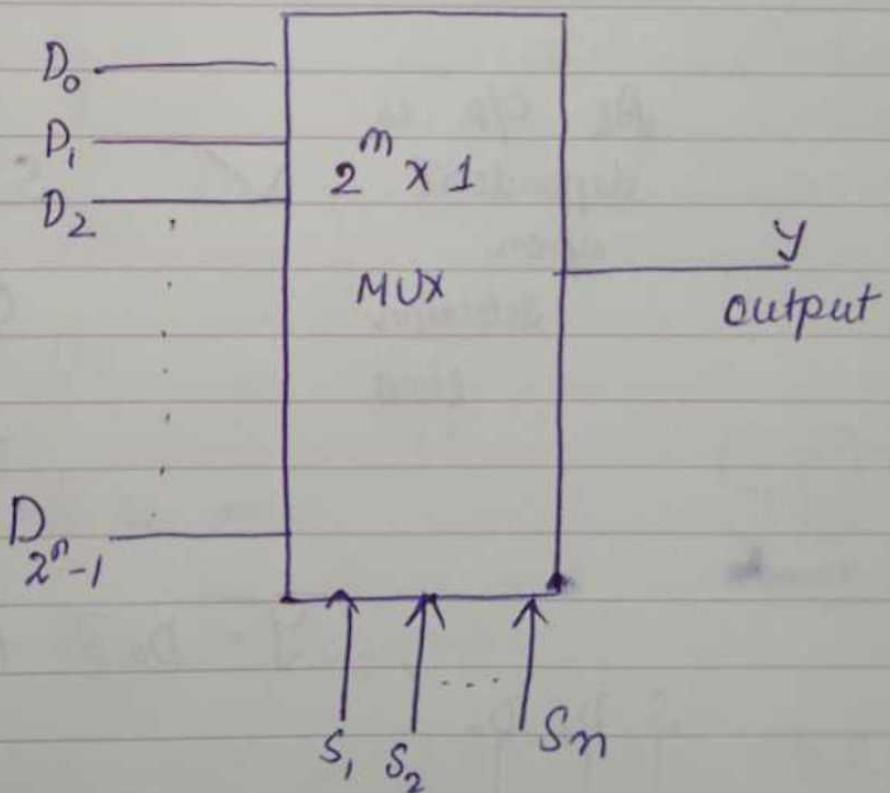↳ For a MUX, there can be 2^n i/p's, 'n' selection lines and only one o/p.



12

THURSDAY • SEPTEMBER

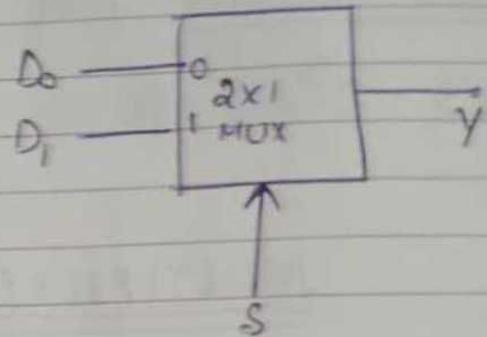 2×1 MUX Design :-jj

D ₀	D ₁	S	Y
----------------	----------------	---	---

X

As O/P is


dependent
upon
selection
line

✓	S	Y
---	---	---

0	D ₀
---	----------------

1	D ₁
---	----------------


$$Y = D_0 \bar{S} + D_1 S$$

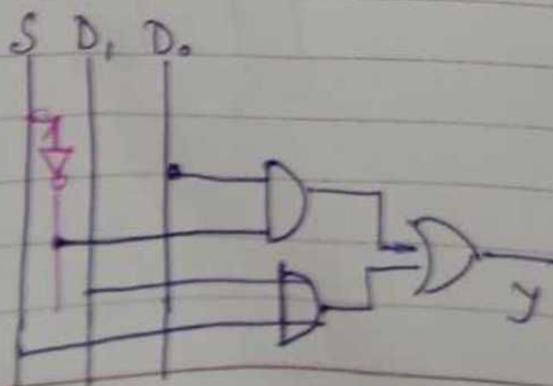

4×1 MUX :-

$$2^n = 4$$

$$\therefore n = 2$$

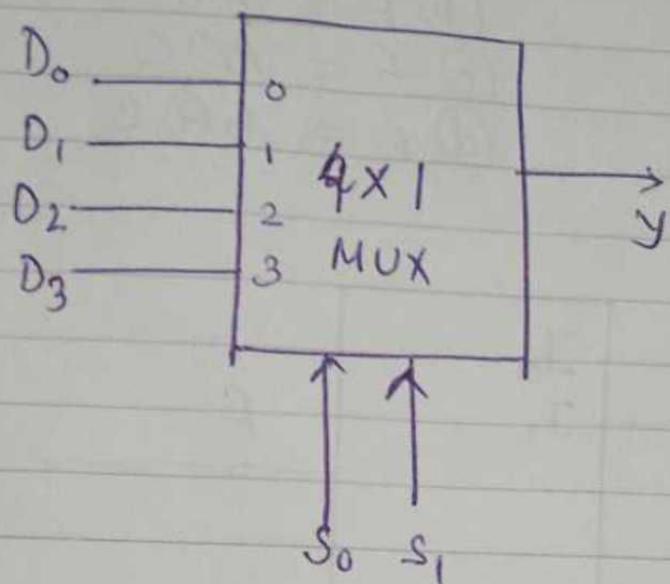

S_0	S_1	y
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3

$$y = D_0 \bar{S}_0 \bar{S}_1 + D_1 \bar{S}_0 S_1 + D_2 S_0 \bar{S}_1 + D_3 S_0 S_1$$

Logic Diagram \rightarrow ?

14



SATURDAY • SEPTEMBER

2019 AUGUST

S	M	T	W	T	F	S
4	5	6	7	8	9	10
11	12	13	14	15	16	17
18	19	20	21	22	23	24
25	26	27	28	29	30	31

Q1 The logic realized by the circuit shown in the figure is -

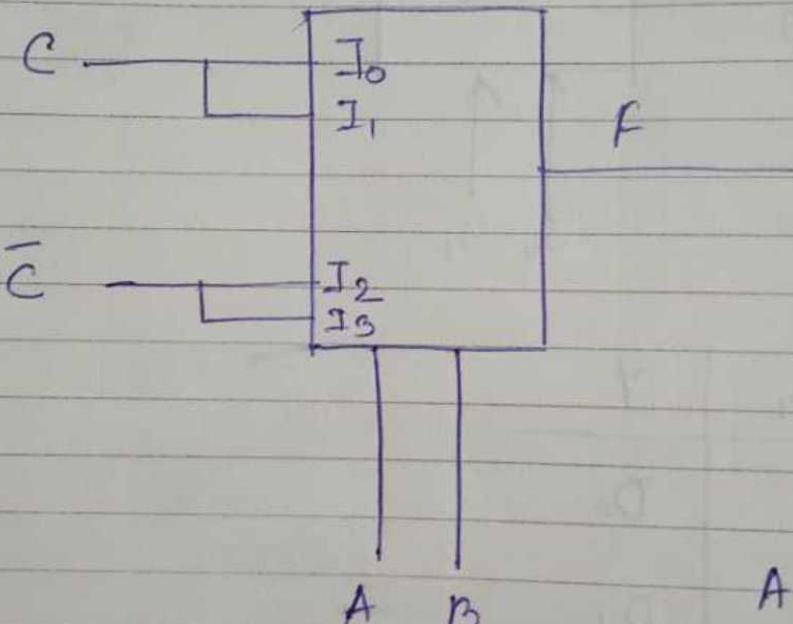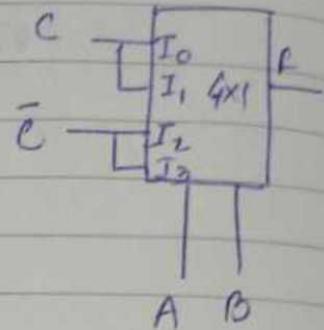- (a) $F = A \odot C$
- (b) $F = A \oplus C$
- (c) $F = B \odot C$
- (d) $F = B \oplus C$



A	B	F
0	0	C
0	1	C
1	0	$\oplus_2 \bar{C}$
1	1	\bar{C}

15

SUNDAY


$$\begin{aligned}
 F &= C\bar{A}\bar{B} + C\bar{A}B + \bar{C}A\bar{B} + \bar{C}AB \\
 &= C\cancel{\bar{A}} C\bar{A} + \bar{C}A \\
 &= A \oplus B
 \end{aligned}$$

OCTOBER - 2019						
M	T	W	T	F	S	S
1	2	3	4	5	6	
8	9	10	11	12	13	
15	16	17	18	19	20	
22	23	24	25	26	27	
29	30	31				

SEPTEMBER • MONDAY

16

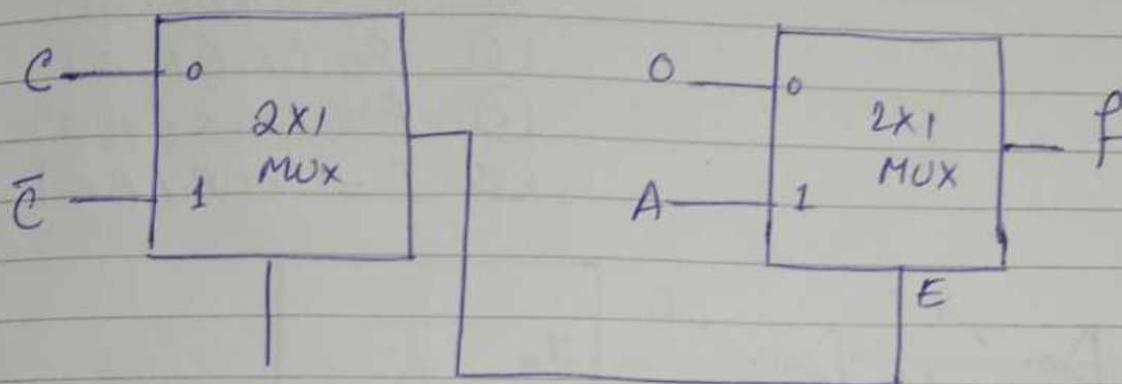Q2. The Boolean 'f' implemented in the figure using two input multiplexers is



P

(a) $A\bar{B}C + A\bar{B}\bar{C}$

(b) $ABC + A\bar{B}\bar{C}$

(c) $\bar{A}BC + \bar{A}\bar{B}\bar{C}$

(d) $\bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C}$

1st MUX2nd MUX

B	E
0	C
1	\bar{C}

E	f
0	0
1	A

$$E = CB + \bar{C}B$$


$$\begin{aligned} f &= AE \\ &= A(CB + \bar{C}B) \\ &= A\bar{B}C + AB\bar{C} \end{aligned}$$

TUESDAY • SEPTEMBER

11	12	13	14	15	16
18	19	20	21	22	23
25	26	27	28	29	30

Q3. The logic function implemented by the circuit below is —

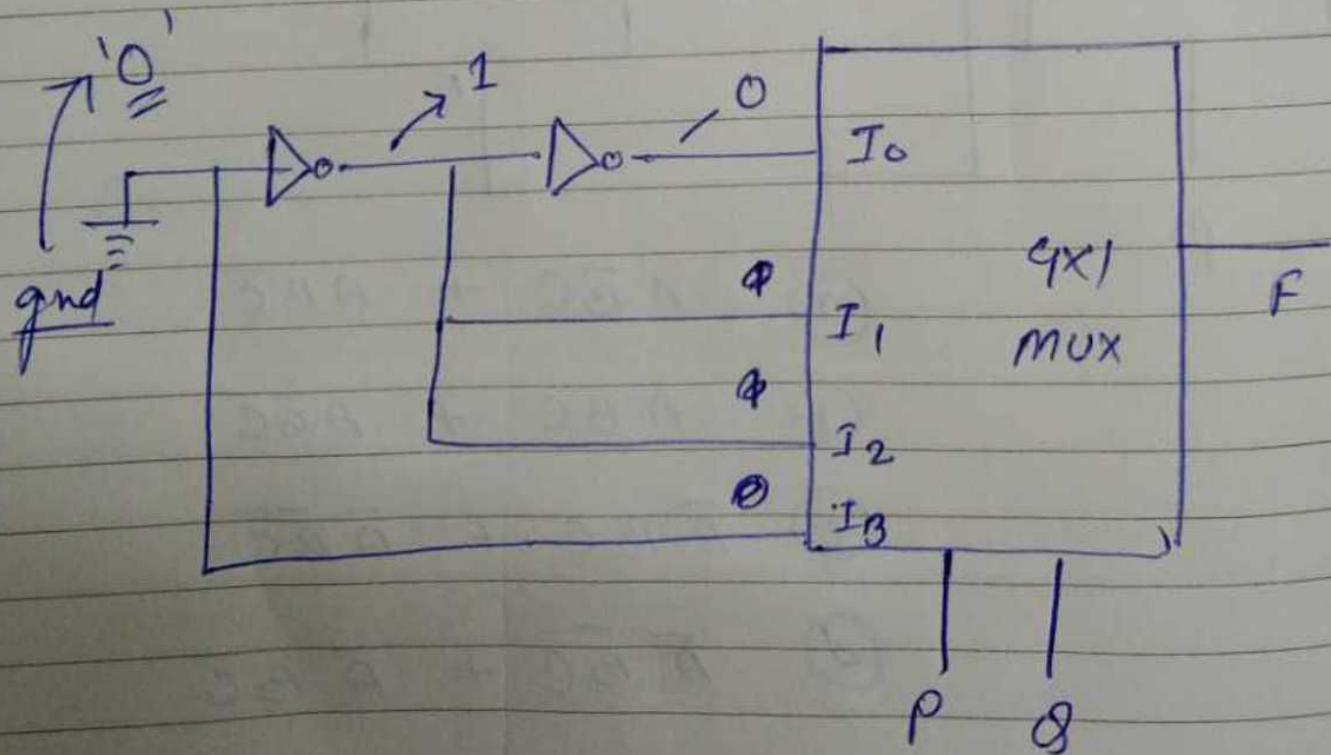- (a) $F = \text{AND}(P, Q)$
- (b) $P = \text{OR}(P, Q)$
- (c) $F = \text{XNOR}(P, Q)$
- (d) $F = \text{XOR}(P, Q)$



OCTOBER						
M	T	W	T	F	S	S
1	2	3	4	5	6	7
8	9	10	11	12	13	14
15	16	17	18	19	20	21
22	23	24	25	26	27	28
29	30	31				


SEPTEMBER • WEDNESDAY

18

DEMULTIPLEXERS (DEMUX)

- 8 ↳ one I/P and many O/Ps.
- 9 ↳ Reverse operation of MUX.
- 10 ↳ Also called as Data Distributor.
- 11 ↳ Demux is a combinational ckt.

MUX	Demux
2:1 / 2x1	1:2 / 2x1
8:1 / 8x1	⊗ 1:8
4:1	⊗ 1:4

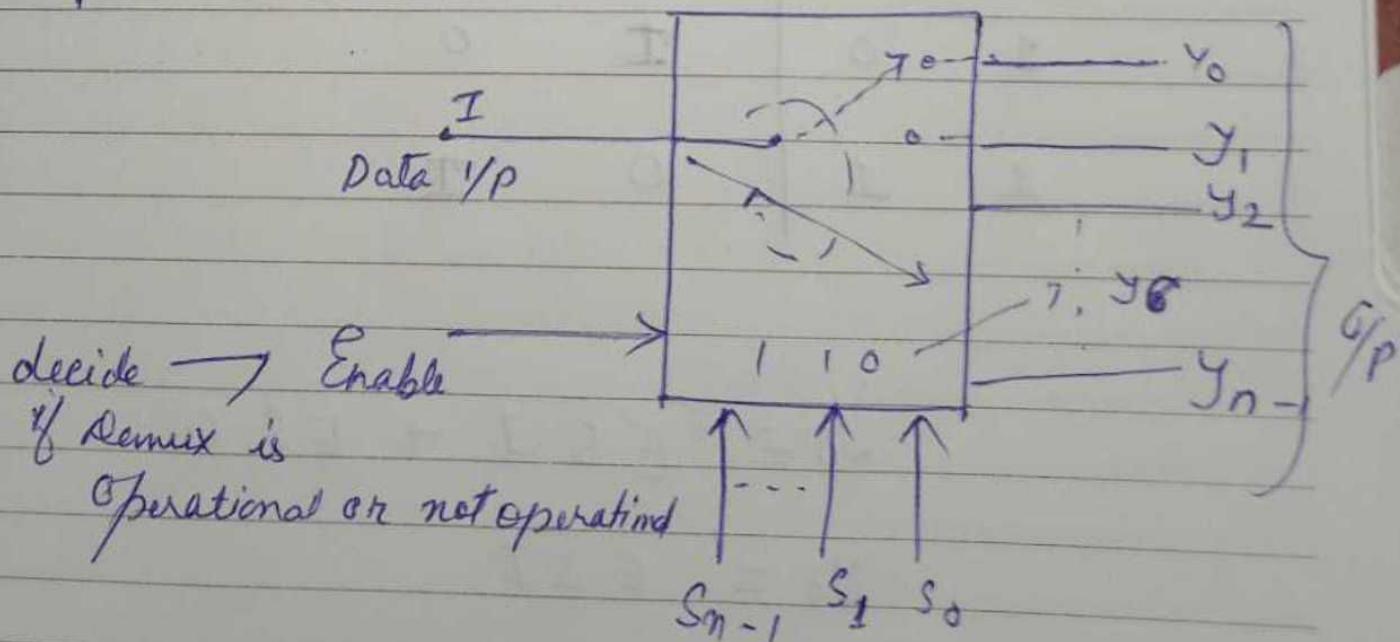

Select line '110' then (c) the data I/P will go to Y_G .

OCTOBER


NOVEMBER

19

THURSDAY • SEPTEMBER

4	5	6	7
11	12	13	14
18	19	20	21
25	26	27	28

1 : 2 Demux

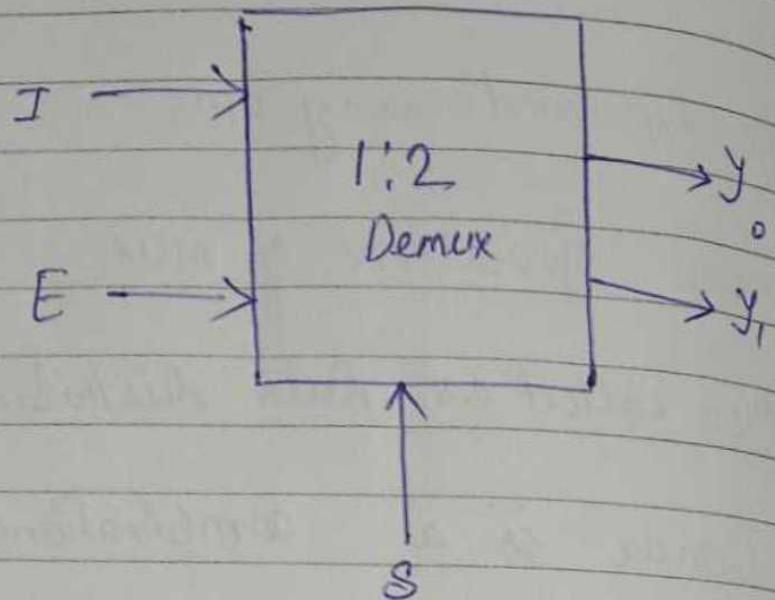

E	S	y_0	y_1
0	0	0	0
0	1	0	0
1	0	1	0
1	1	0	1

$$y_0 = \bar{E} \bar{S} \cdot I + E S \cdot 0$$

$$y_0 = \bar{E} \bar{S} I$$

$$y_1 = E S I$$

8 9 10 11 12 13
14 15 16 17 18 19 20
21 22 23 24 25 26 27
28 29 30 31

SEPTEMBER • FRIDAY

20

logic Diagram

